
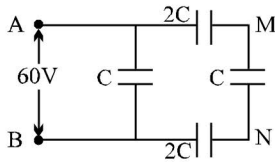


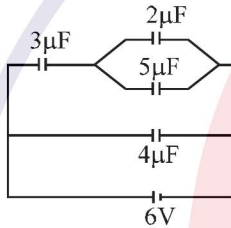
1. In the circuit shown, a potential difference of 60V is applied across AB. The potential difference between the point M and N is :-




- (1) 10 V (2) 15 V  
 (3) 20 V (4) 30 V
2. In the circuit shown in figure, the ratio of charges on  $5\mu\text{F}$  and  $4\mu\text{F}$  capacitor is :-



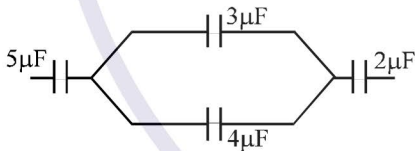- (1) 4/5 (2) 3/5  
 (3) 3/8 (4) 1/2
3. If charge on left plate of the  $5\mu\text{F}$  capacitor in the circuit segment shown in the figure is  $-20\mu\text{C}$ , the charge on the right plate of  $3\mu\text{F}$  capacitor is :-




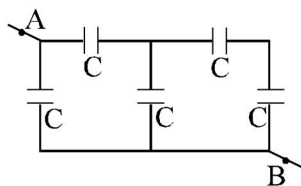- (1)  $+8.57\mu\text{C}$  (2)  $-8.57\mu\text{C}$   
 (3)  $+11.42\mu\text{C}$  (4)  $-11.42\mu\text{C}$
4. What is the equivalent capacitance of the system of capacitors between A & B as shown in the figure.




- (1)  $\frac{7}{6}C$  (2)  $1.6C$  (3)  $C$  (4) None

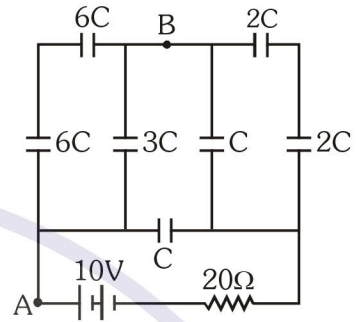5. For the circuit shown here, the potential difference between points A and B is




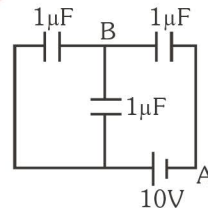
- (1) 2.5 V (2) 7.5 V  
 (3) 10 V (4) Zero
6. If potential of A is 10V, then potential of B is -





- (1)  $25/3V$  (2)  $50/3V$   
 (3)  $100/3V$  (4)  $50V$
7. A parallel plate capacitor has an electric field of  $10^5\text{V/m}$  between the plates. If the charge on the capacitor plate is  $1\mu\text{C}$ , then the force on each capacitor plate is
- (1) 0.1Nt (2) 0.05Nt  
 (3) 0.02Nt (4) 0.01Nt
8. A conducting body 1 has some initial charge  $Q$ , and its capacitance is  $C$ . There are two other conducting bodies, 2 and 3, having capacitances :  $C_2 = 2C$  and  $C_3 \rightarrow \infty$ . Bodies 2 and 3 are initially uncharged. "Body 2 is touched with body 1. Then, body 2 is removed from body 1 and touched with body 3, and then removed." This process is repeated  $N$  times. Then, the charge on body 1 at the end must be
- (1)  $Q/3^N$  (2)  $Q/3^{N-1}$   
 (3)  $Q/N^3$  (4) None

# CAPACITOR

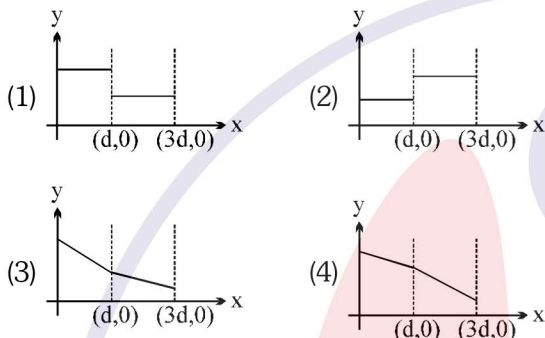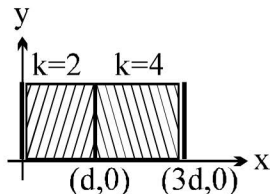9. A parallel plate capacitor has two layers of dielectric as shown in figure. This capacitor is connected across a battery. The graph which shows the variation of electric field (E) and distance (x) from left plate is



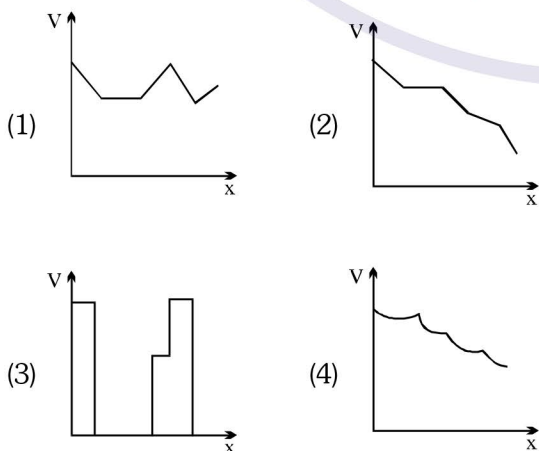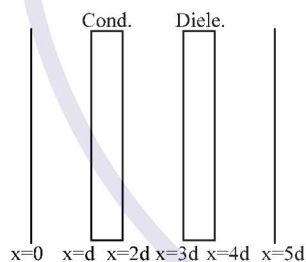
10. The distance between plates of a parallel plate capacitor is  $5d$ . Let the positively charged plate is at  $x=0$  and negatively charged plate is at  $x=5d$ . Two slabs one of conductor and other of a dielectric of equal thickness  $d$  are inserted between the plates as shown in figure. Potential versus distance graph will look like :



11. Three capacitors  $2\ \mu\text{F}$ ,  $3\ \mu\text{F}$  and  $5\ \mu\text{F}$  can withstand voltages to  $3\text{V}$ ,  $2\text{V}$  and  $1\text{V}$  respectively. Their series combination can withstand a maximum voltage equal to


- (1)  $5\text{ Volts}$  (2)  $(31/6)\text{ Volts}$   
 (3)  $(26/5)\text{ Volts}$  (4) None

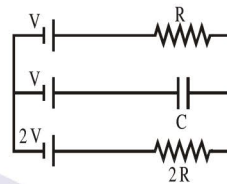12. In the given circuit, with steady current the potential drop across the capacitor must be :-



- (1)  $V$  (2)  $\frac{V}{2}$  (3)  $\frac{V}{3}$  (4)  $\frac{2V}{3}$

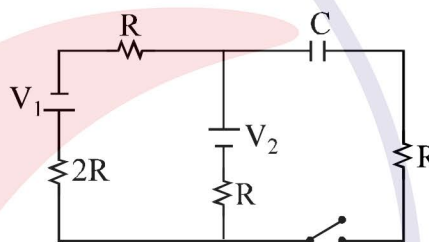13. In the transient circuit shown the time constant of the circuit is :




- (1)  $\frac{5}{3}RC$  (2)  $\frac{5}{2}RC$  (3)  $\frac{7}{4}RC$  (4)  $\frac{7}{3}RC$

14. A parallel plate capacitor is connected to a battery. The quantities charge, voltage, electric field and energy associated with the capacitor are given by  $Q_0$ ,  $V_0$ ,  $E_0$  and  $U_0$  respectively. A dielectric slab is introduced between plates of capacitor but battery is still in connection. The corresponding quantities now given by  $Q$ ,  $V$ ,  $E$  and  $U$  related to previous ones are

- (1)  $Q > Q_0$  (2)  $V > V_0$   
 (3)  $E > E_0$  (4)  $U < U_0$

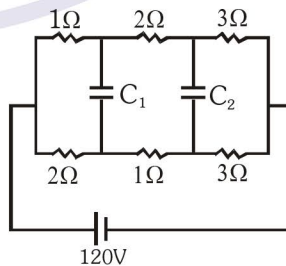
15. In the circuit shown in figure  $C_1 = C_2 = 2\ \mu\text{F}$ . Then charge stored in



- (1) capacitor  $C_1$  is zero  
 (2) capacitor  $C_2$  is zero  
 (3) both capacitor is zero  
 (4) capacitor  $C_1$  is  $40\ \mu\text{C}$


# CAPACITOR

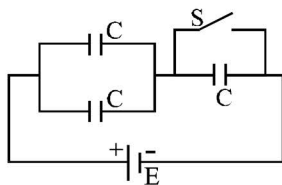16. In the circuit shown, each capacitor has a capacitance  $C$ . The emf of the cell is  $E$ . If the switch  $S$  is closed




- (1) positive charge will flow out of the positive terminal of the cell
- (2) positive charge will enter the positive terminal of the cell
- (3) the amount of charge flowing through the cell will be  $CE$ .
- (4) the amount of charge flowing through the cell will be  $4/3 CE$ .

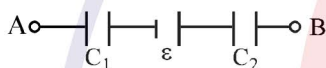17. A circuit shown in the figure consists of a battery of emf  $10\text{ V}$  and two capacitance  $C_1$  and  $C_2$  of capacitances  $1.0\ \mu\text{F}$  and  $2.0\ \mu\text{F}$  respectively. The potential difference  $V_A - V_B$  is  $5\text{ V}$




- (1) charge on capacitor  $C_1$  is equal to charge on capacitor  $C_2$
- (2) Voltage across capacitor  $C_1$  is  $5\text{ V}$ .
- (3) Voltage across capacitor  $C_2$  is  $10\text{ V}$
- (4) Energy stored in capacitor  $C_1$  is two times the energy stored in capacitor  $C_2$ .

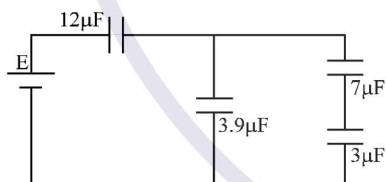18. Four capacitors and a battery are connected as shown. The potential drop across the  $7\ \mu\text{F}$  capacitor is  $6\text{ V}$ . Then the :




- (1) potential difference across the  $3\ \mu\text{F}$  capacitor is  $10\text{ V}$
- (2) charge on the  $3\ \mu\text{F}$  capacitor is  $42\ \mu\text{C}$
- (3) e.m.f. of the battery is  $30\text{ V}$
- (4) potential difference across the  $12\ \mu\text{F}$  capacitor is  $10\text{ V}$ .

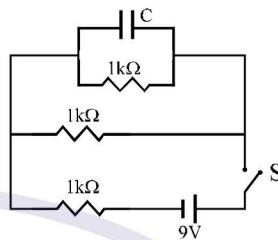19. A capacitor  $C = 100\ \mu\text{F}$  is connected to three resistor each of resistance  $1\ \text{k}\Omega$  and a battery of emf  $9\text{ V}$ . The switch  $S$  has been closed for long time so as to charge the capacitor. When switch  $S$  is opened, the capacitor discharges with time constant



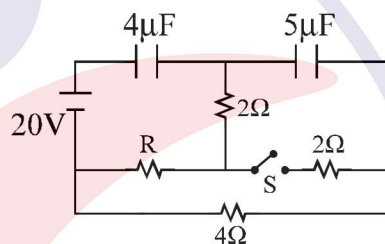- (1)  $33\text{ ms}$
  - (2)  $5\text{ ms}$
  - (3)  $3.3\text{ ms}$
  - (4)  $50\text{ ms}$
20. Find heat produced on closing the switch  $S$



- (1)  $0.0002\text{ J}$
- (2)  $0.0005\text{ J}$
- (3)  $0.00075$
- (4) zero

## ANSWER KEY

## Exercise-I

Que.	1	2	3	4	5	6	7	8	9	10
Ans.	4	3	1	2	1	2	2	1	1	2
Que.	11	12	13	14	15	16	17	18	19	20
Ans.	2	3	3	1	2,4	1,4	1,4	2,3,4	4	4