

# SEMICONDUCTOR

## THEORY

### Introduction

The word 'electronics' is derived from electron+dynamics which means the study of the behaviour of an electron under different conditions of externally applied fields.

This field of science deals with electronic devices and their utilization. An electronic device is a device in which conduction takes place by the movement of electron - through a vacuum, a gas or a semiconductor.

Some familiar devices are : (i) Rectifier (ii) Amplifier (iii) Oscillator etc.

### Application of Electronics


Communication	Entertainment	Defence	Medical
Telephone	TV Broadcast	Radar	X-rays
Telegraph	Radio Broadcast	Guided missiles	Electro cardio graph (E.C.G.)
Mobile phone	VCR, VCD		CRO display
FAX, FM mic			Electro Engio Graph (E.E.G.)

Main application of electronics is computer which is used in every field.

All electronics equipment's required D.C. supply for operation (not A.C. supply).

### Classification of Materials and Energy Band Theory

#### Classification of Solids

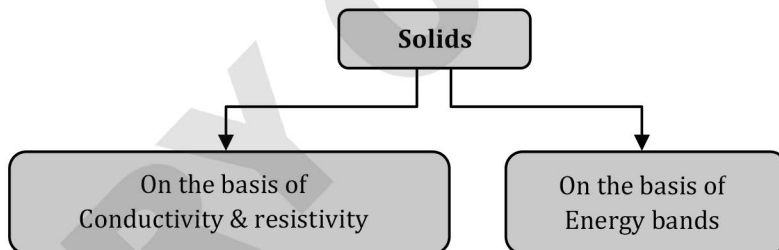

**On the basis of conductivity & resistivity:** It have three types;

1. Conductors
2. Insulators
3. Semiconductors


Conductors	Insulators	Semiconductors
Abundance of free $e^-$	Very few free $e^-$	Few free $e^-$
High conductivity ( $\sigma \sim 10^2 - 10^8 \text{ S m}^{-1}$ )	Low conductivity ( $\sigma \sim 10^{-11} - 10^{-19} \text{ S m}^{-1}$ )	Intermediate conductivity ( $\sigma \sim 10^5 - 10^{-6} \text{ S m}^{-1}$ )
Low resistivity ( $\rho \sim 10^{-2} - 10^{-8} \Omega\text{m}$ )	High resistivity ( $\rho \sim 10^{11} - 10^{19} \Omega\text{m}$ )	Intermediate resistivity ( $\rho \sim 10^{-5} - 10^6 \Omega\text{m}$ )
Effect of temperature: $T \uparrow R \uparrow \rho \uparrow \sigma \downarrow$	(At very high temperature) $T \uparrow R \downarrow \rho \downarrow \sigma \uparrow$	(At room temperature) $T \uparrow R \downarrow \rho \downarrow \sigma \uparrow$
$\alpha = +ve$	$\alpha = -ve$	$\alpha = -ve$ ( $\alpha = \text{temp. coefficient}$ )
E.g. : Metals	E.g.: Rubber, Wood, Plastic, Diamond etc.	E.g. : Si, Ge, GaAs, CdS, anthracene, Polypyrole, Polyaniline etc
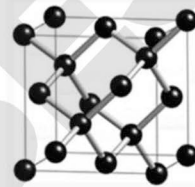
## Energy Bands in Solids

- In isolated atoms the energy levels of electrons are discrete.
- When we draw the energy level diagram of isolated Si atom then we obtain different energy levels corresponding to the energy of different electrons in different orbits.



- However, if an atom belongs to a crystal, then the energy levels are modified.
- Consider a single crystal of silicon having N atoms. Each atom can be associated with a lattice site.
- Electronic configuration of  ${}_{14}\text{Si}$  is  $1s^2, 2s^2, 2p^6, 3s^2, 3p^2$ .



- Therefore interaction of a silicon atom with the neighbouring atom causes change in energy levels of electron.
- This modification is not appreciable in the case of energy levels of electrons in the inner shells (completely filled).
- But in the outermost shells, modification is appreciable because the electrons are shared by many neighbouring atoms.
- So, what used to be the discrete energy levels, now split-up or spread out to form energy bands.

**Valence Band:** This is lower energy band, which contains valence electrons.

This band is either partially or completely filled with electrons but never be empty.

The electrons in this band are not capable of taking part in conduction of current.

**Conduction Band:** This is the higher band containing conduction electrons.

This band is either empty or partially filled with electrons.

Electrons present in this band take part in the conduction of current.

This band is completely empty. Electron is forbid to be in this energy gap.

The minimum energy required to shift an electron from valence band to conduction band is called band gap ( $\Delta E_g$ ).

$$\Delta E_g = (\text{CB})_{\min} - (\text{VB})_{\max}$$


It depends on nature of solid and on the interatomic separation.

It also depends on temperature, but this dependence is very weak.
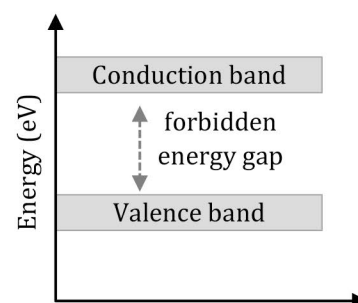
### Band gap or Forbidden Energy gap (FEG) ( $\Delta E_g$ )


$$\Delta E_g = (\text{CB})_{\min} - (\text{VB})_{\max}$$

- It is the energy gap between CB and VB.
- It is also called forbidden energy gap because free electrons cannot exist in this gap.
- Width of forbidden energy gap depends upon the nature of substance.
- Width is more, then valence electrons are strongly attached with nucleus.
- Width of forbidden energy gap is represented in eV.
- As temperature increases forbidden energy gap decreases (very slightly).


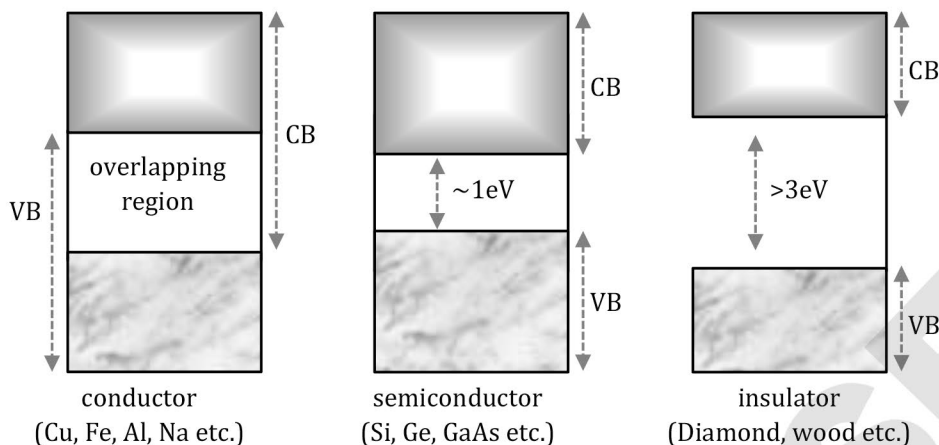
## Classification of solids According to Energy Band Theory

According to energy band theory solids are conductor, semiconductor and insulator :



**Conductor:** In some solids conduction band and valence band are overlapped so there is no band gap between them, it means  $\Delta E_g = 0$ . Due to this a large number of electrons are available for electrical conduction and therefore its resistivity is low ( $\rho = 10^{-2} - 10^{-8} \Omega\text{-m}$ ) and conductivity is high [ $\sigma = 10^2 - 10^8 (\Omega\text{-m})^{-1}$ ]

Such materials are called conductors. For example, gold, silver, copper etc.

**Insulator:** In some solids energy gap is large ( $E_g > 3 \text{ eV}$ ). So, in conduction band there are no electrons and no electrical conduction is possible. Here energy gap is so large that electrons cannot be easily excited from the valence band to conduction band by any external energy (electrical, thermal or optical).

Such materials are called as "insulator". Their  $r > 10^{11} \text{ W-m}$  and  $s < 10^{-11} (\text{W-m})^{-1}$

**Semiconductor:** In some solids a finite but small band gap exists ( $E_g < 3\text{eV}$ ). Due to this small band gap some electrons can be thermally excited to "conduction band". These thermally excited electrons can move in conduction band and can conduct current. Their resistivity and conductivity both are in medium range,  $\rho; 10^{-5} - 10^6 \Omega\text{-m}$  and  $\sigma; 10^{-6} - 10^5 \Omega\text{-m}^{-1}$ .

### Example of semiconducting materials


Elemental semiconductor : Si and Ge


- Compound semiconductor
- Inorganic : CdS, GaAs, CdSe, InP etc.
  - Organic : Anthracene, Doped pthalocyanines etc.
  - Organic polymers : Poly pyrrole, Poly aniline, polythiophene
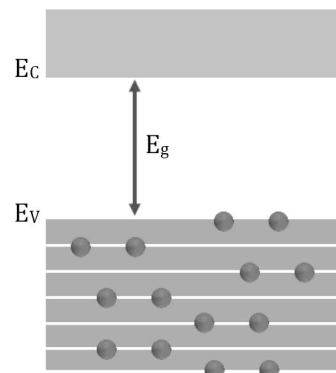
### Intrinsic Semiconductors

Semiconductors in their purest form. Free from any type of impurity All the covalent bonds are complete, No free electrons. Valence bands are completely filled. Conduction bands are complete empty. It behaves as perfect insulator.

Some of the covalent bonds are broken due to thermal energy.



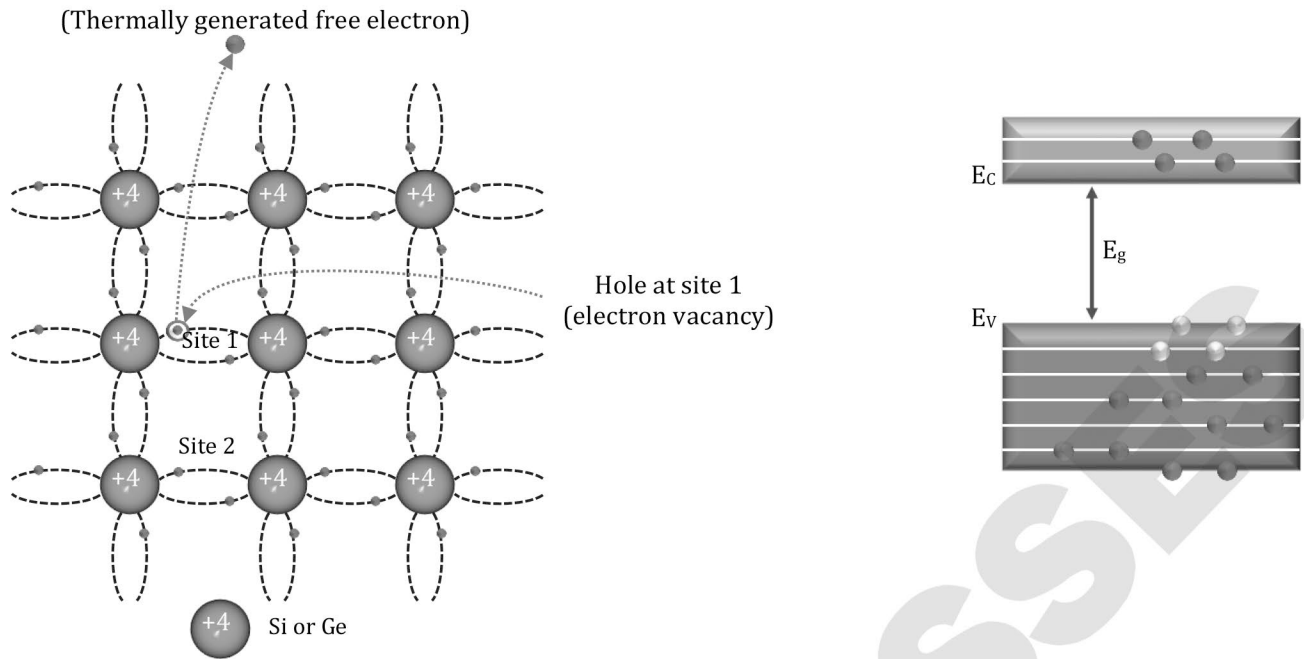

On receiving an additional energy, one of the electrons from a covalent bond breaks and is free to move in the crystal lattice.

While coming out of the covalent bond, it leaves behind a vacancy named 'hole'. This process is called Electron-hole pair generation.

**In intrinsic semiconductor, the number of thermally generated electrons always equals the number of holes.**

$n_e$  = free electron concentration,  $n_h$  = hole concentration

$$n_e = n_h = n_i$$

$$\text{Total Current} = I_h + I_e$$

Valence Band Current  $I_h$ , Conduction Band Current  $I_e$

### Conductivity ( $\sigma$ )

$$\sigma = e (n_e \mu_e + n_h \mu_h) = \sigma_e + \sigma_h$$

Where,  $\sigma_e = \mu_e n_e e$  &  $\sigma_h = \mu_h n_h e$

### Properties of Semiconductor

Negative temperature coefficient ( $\alpha$ ), with increase in temperature resistance decreases.

Crystalline structure with covalent bonding [Face centred cubic (FCC)].


Conduction properties may change by adding small impurities.

Position in periodic table  $\rightarrow$  IV group (Generally)

Forbidden energy gap (0.1 eV to 3 eV)



Charge carriers : electron and hole.

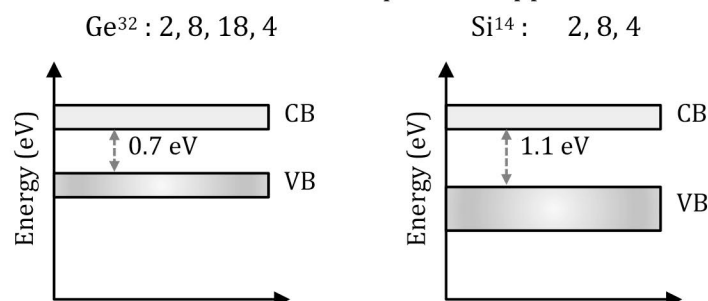There are many semiconductors but few of them have practical application in electronics like





## Effect of temperature

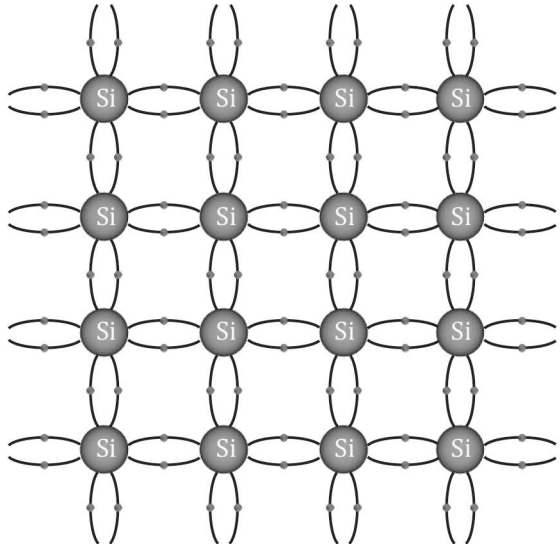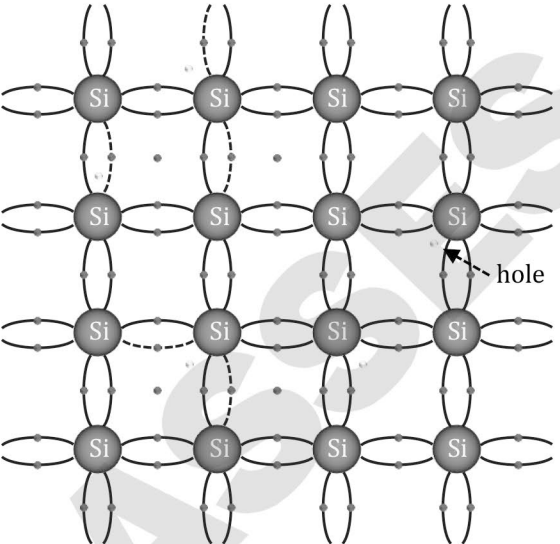
At absolute zero kelvin temperature at this temperature covalent bonds are very strong and there are no free electrons and semiconductor behaves as perfect insulator.	Above absolute temperature with increase in temperature some covalent bonds are broken and few valence electrons jump to conduction band and hence it behaves as poor conductor.
 <p style="text-align: center;">at 0k</p> <p>Valence band fully filled      conduction band fully empty</p>	 <p style="text-align: center;">at higher temperature</p> <p>Valence band partially empty      conduction band partially filled</p>

## Concept of electron current and hole current

In conductors current is caused by only motion of electrons but in semiconductors current is caused by both electrons in conduction band and holes in valence band.

Current that is caused by electron motion is called electron current and current that is caused by hole motion is called hole current. Electron is a negative charge carrier whereas hole is a positive charge carrier. At absolute zero temperature intrinsic semiconductor behaves as insulator. However, at room temperature the electrons present in the outermost orbit absorb thermal energy. When the outermost orbit electrons get enough energy then they will break bonding with the nucleus of atom and jumps in to conduction band. The electrons present in conduction band are not attached to the nucleus of an atom so they are free to move.

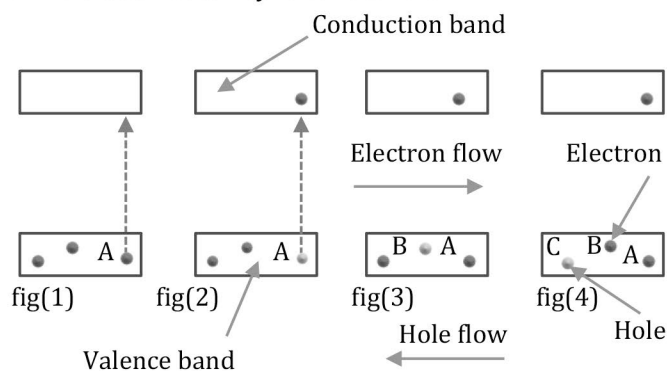
When the valence electron moves from valence band to the conduction band a vacancy is created in the valence band where electron left. Such vacancy is called hole.


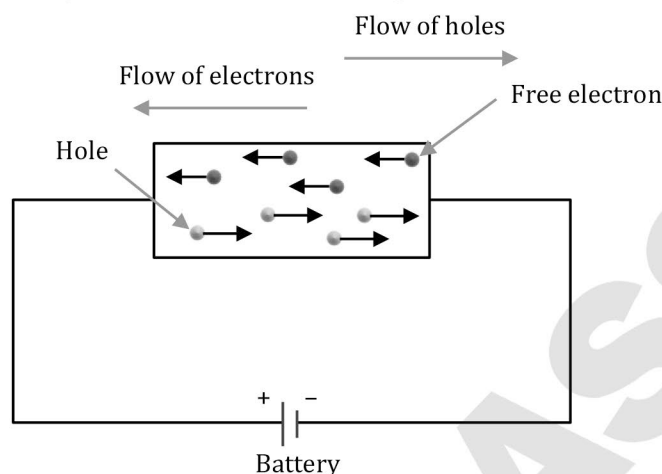
### Conduction in intrinsic semiconductor

The process of conduction in intrinsic semiconductor is shown in below fig. In the below fig, an intrinsic semiconductor is connected to a battery.

Here, positive terminal of battery is connected to one side and negative terminal of the battery is connected to other side. As we know like charges repel each other and opposite charges attract each other. In the similar way negative charge carriers (electrons) are attracted towards the positive terminal of battery and positive charge carriers (holes) attracted towards the negative terminal of battery.



Electrons will experience a attractive force from the positive terminal, so they move towards the positive terminal of the battery by carrying the electric current. Similarly, holes will experience a attractive force from the negative terminal, so they moves towards the negative terminal of the battery by carrying the electric current. Thus, in a semiconductor electric current is carried by both electrons and holes.

In intrinsic semiconductor the number of free electrons in conduction band is equal to the number of holes in valence band. The current caused by electrons and holes is equal in magnitude.

The total current in intrinsic semiconductor is the sum of hole and electron current.

$$I = I_{\text{hole}} + I_{\text{electron}}$$

### Extrinsic Semiconductors

#### n-type and p-type Semiconductor

The conductivity of an intrinsic semiconductor depends on its temperature, but at room temperature its conductivity is very low. As such, no important electronic devices can be developed using these semiconductors.

Hence there is a necessity of improving their conductivity. This can be done by making use of impurities.

When a small amount, say, a few parts per million (ppm), of a suitable impurity is added to the pure semiconductor, the conductivity of the semiconductor is increased manifold. Such materials are known as extrinsic semiconductors or impurity semiconductors.


Extrinsic semiconductors are semiconductors that are doped with specific impurities. The impurity modifies the electrical properties of the semiconductor and makes it more suitable for electronic devices such as diodes and transistors.

The deliberate addition of a desirable impurity is called doping and the impurity atoms are called dopants. Such a material is also called a doped semiconductor.

Intrinsic Semiconductor + Dopants = Extrinsic Semiconductor
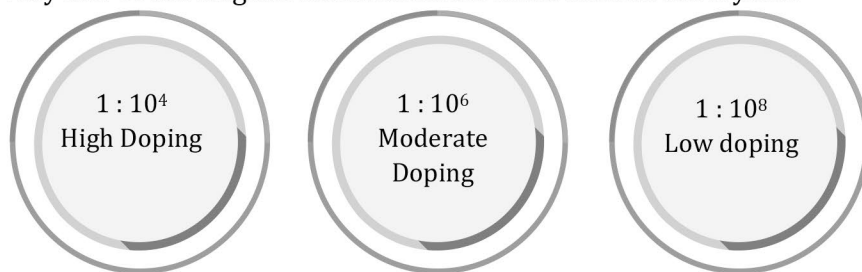
## Properties of Dopants

It occupies only a very few of the original semiconductor atom sites in the crystal.






It should not distort the original pure semiconductor lattice.

Sizes of the dopant and the semiconductor atoms should be nearly the same.

It should give away holes or electron for conduction very easily.
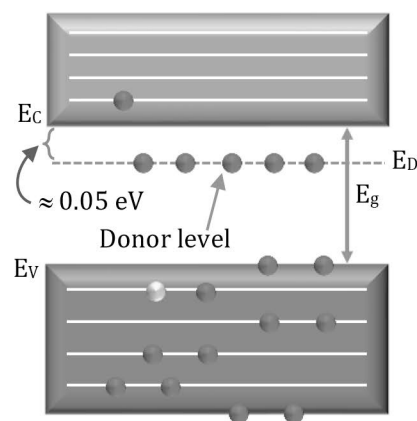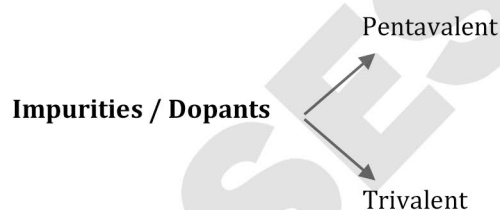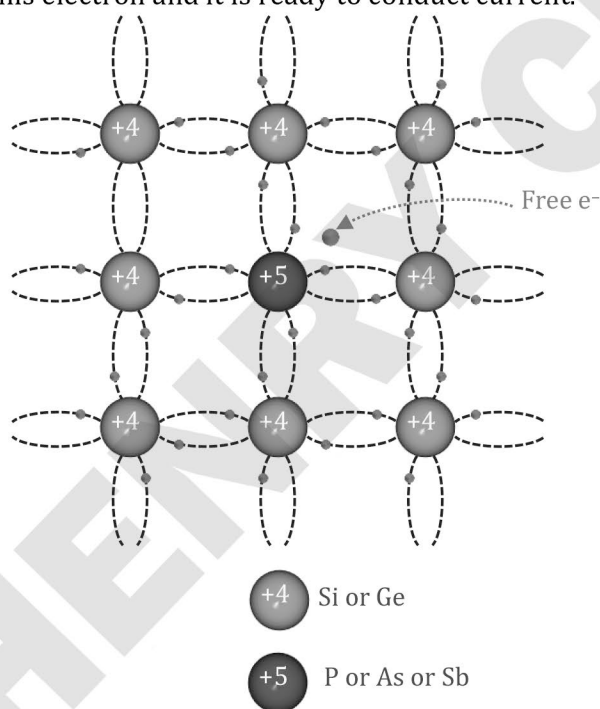
### 1. n-type semiconductor

When Si or Ge is doped with a pentavalent impurity, n-type semiconductor is formed. The force of attraction between this mobile electron and the positively charged (+5) impurity ion is weakened. So, such electrons from impurity atoms will have energies slightly less than the energies of the electrons in the conduction band. The energy required to detach the fifth loosely bound electron is only of the order of 0.05 eV for Si and 0.01 eV for Ge. A small amount of energy provided due to thermal agitation is sufficient to detach this electron and it is ready to conduct current.



Free electron concentration is mainly decided by the donor impurity concentration. ( $n_e = N_D$ )

The number of holes decreases because of increase in rate of recombination.



Free electrons are the majority carriers and holes are the minority carriers. ( $n_e \gg n_h$ )

Total current in semiconductor is mainly due to electron current,  $I = I_e + I_h \approx I_e$

Overall semiconductor is still neutral.
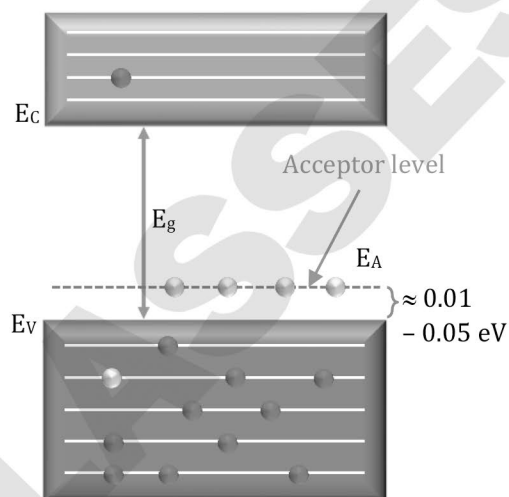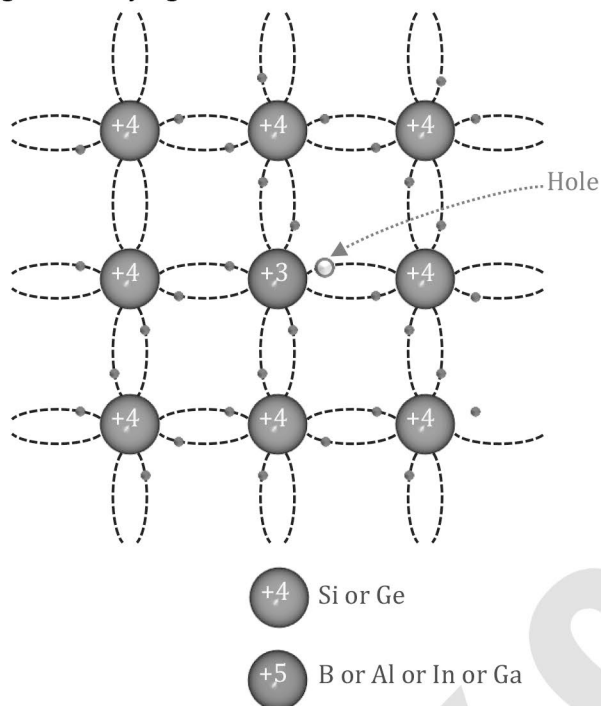
## 2. P-type semiconductor

When Si or Ge is doped with a trivalent impurity, p-type semiconductor is formed. The vacancy of trivalent impurity may be filled with an electron from neighbouring atom, creating a hole in that position from where the electron jumped. The acceptor impurity produces an energy level just above the valence band. The energy difference between the acceptor energy level and the top of the valence band is much smaller (0.01 eV) than the band gap. Electrons from the valence band can, easily move into the acceptor level by being thermally agitated.



Hole concentration is mainly decided by the acceptor impurity concentration. ( $n_h = N_A$ )

The number of electrons further decreases due to increase in rate of recombination.

Holes are the majority carriers and free electrons are the minority carriers. ( $n_h \approx n_e$ )

Total current in semiconductor is mainly due to hole current,  $I = I_e + I_h \approx I_h$

Overall semiconductor is still neutral.

Intrinsic Semiconductor	N-type (Pentavalent impurity)	P-type (Trivalent impurity)
<p>1.</p>	<p>donor impurity level</p>	<p>acceptor impurity level</p>
<p>2.</p>	<p>free electron positive donor ion</p>	<p>hole negative acceptor ion</p>

3. Current is due to both electrons and holes	Mainly due to electrons	Mainly due to holes
4. $n_e = n_h = n_i$	$n_e \gg n_h$ ( $N_D \approx n_e$ )	$n_h \gg n_e$ ( $N_A \approx n_h$ )
5. $I = I_e + I_h$	$I \approx I_e$	$I \approx I_h$
6. Entirely neutral	Entirely neutral	Entirely neutral
7. Quantity of electrons and holes are equal	Majority - Electrons Minority - Holes	Majority - Holes Minority - Electrons

### Mass action law

At room temperature, most of the acceptor atoms get ionised leaving holes in the valence band. Thus at room temperature the density of holes in the valence band is predominantly due to impurity in the extrinsic semiconductor.

“Rate of generation of charge carriers is equal to rate of recombination of charge carriers.”

$$n_e n_h = n_i^2$$

**Note:**  $n_i$  depends only on the nature of semiconductor material and temperature, it does not depend on the doping level.

### Illustration 1:

Pure Si at 300 K has equal electron ( $n_e$ ) and hole ( $n_h$ ) concentrations of  $1.5 \times 10^{16} \text{ m}^{-3}$ . Doping by indium  $n_h$  increases to  $3 \times 10^{22} \text{ m}^{-3}$ . Calculate  $n_e$  in the doped Si.

### Solution:

For a doped semi-conductor in thermal equilibrium  $n_e n_h = n_i^2$  (Law of mass action)

$$n_e = \frac{n_i^2}{n_h} = \frac{(1.5 \times 10^{16})^2}{3 \times 10^{22}} = 7.5 \times 10^9 \text{ m}^{-3}$$

### Doping

Doping is the mixing of impure atoms in a pure semiconductor material. Here the impure atoms refer to the atoms that are different from the pure semiconductor. The most commonly used impure atoms are Boron (B), Aluminum (Al), Arsenic (As), Phosphorus (P) etc.

**Necessity of Doping:** The Conductivity of semiconductors is very poor at room temperature. To get a significant amount of conductivity we need to increase the temperature of the semiconductor to a high value. But it is practically impossible to use the semiconductor devices at a very high temperatures above  $50^\circ\text{C}$ .


Now, doping can increase the conductivity of semiconductors by a significant amount even at room temperature. At this one can use semiconductor devices comfortably at room temperature.

So, we need the doping in semiconductor materials to increase their conductivity without increasing the temperature which enables us to use semiconductor devices at room temperature.


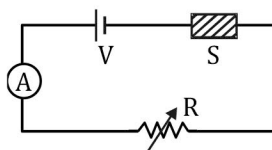
## BEGINNER'S BOX-1

- The diagram shows a piece of pure semiconductor  $S$ , in series with a variable resistor  $R$ , and a source of constant voltage  $V$ . Would you increase or decrease the value of  $R$  to keep the reading of ammeter (A) constant, when semiconductor  $S$  is heated? Give reason.



- Pure Si at 300 K has equal electron  $n_e$  and hole  $n_h$  concentration of  $1.5 \times 10^{16}/\text{m}^3$ . Doping by indium increases  $n_h$  to  $4.5 \times 10^{22}/\text{m}^3$ . Calculate  $n_e$  in doped silicon.
- Suppose a pure Si crystal has  $5 \times 10^{28}$  atoms  $\text{m}^{-3}$ . It is doped by 1 ppm concentration of pentavalent As. Calculate the number of electrons and hole. (Given that  $n_i = 1.5 \times 10^{16} \text{m}^{-3}$ .)
- For given semiconductor contribution of current due to electron and hole is in ratio 3/1 and the ratio of drift velocity for electron and hole is 5/2, then calculate the ratio of electron to hole concentration.

## P-N Junction Diode & Diode Formation

When a p-type semiconductor is joined to a n-type semiconductor such that the crystal structure remains continuous at the boundary, the resulting arrangement is called a p-n junction diode.

**There are two important processes in the p-n junction.**

1. Diffusion
2. Drift

### 1. Diffusion


It occurs for majority charge carriers due to concentration gradient. Holes diffuses from p-side to n-side of the junction. Electrons diffuses from n-side to p-side of the junction. Direction of diffusion current is from p-side to n-side.

### 2. Drift

It occurs for minority charge carriers due to electric field in the depletion region. Electron drift from p-side to the n-side of the junction. Holes drift from n-side to the p-side of the junction.

Electrons and holes drift to their respective majority sides. Direction of drift current is from n to p, opposite to that of diffusion current. Initially, diffusion current is large and drift current is small. As the diffusion process continues, the electric field strength increases and hence drift current. This process continues until the diffusion current equals the drift current. Thus, a p-n junction is formed. In a p-n junction under equilibrium there is no net current. It means  $|I_{\text{Drift}}| = |I_{\text{Diffusion}}|$

### Depletion Width

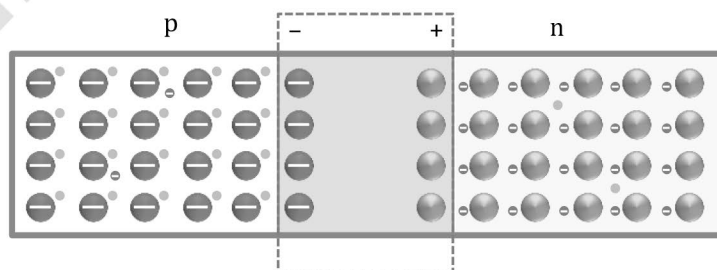


Width of Depletion region  $\sim 0.1 \mu\text{m}$

It depends on temperature, doping and type of material  $\text{width} \propto \frac{1}{\sqrt{\text{Doping}}}$
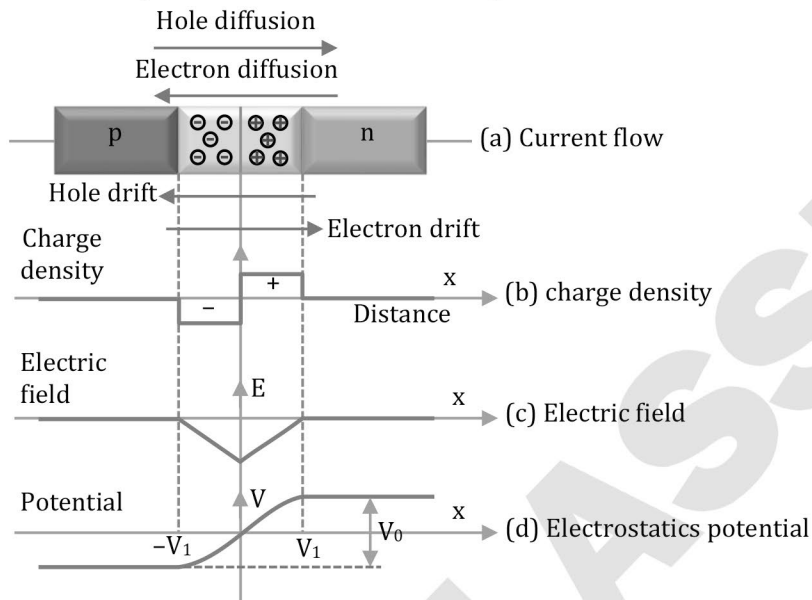
### Barrier Potential or Built-in Potential

An electric field is set up from n-side to p-side. Thus n-region have higher potential than p-region. The difference in potential between p and n regions across the junction makes it difficult for the holes and electrons to move across the junction. This acts as a barrier and hence called 'potential barrier'. Depends on temperature, doping and nature of semiconductor material. The potential barrier opposes the motion of the majority carriers and helps the movement of minority carriers.



### Types of Biasing

A semiconductor diode is basically a p-n junction with metallic contacts provided at the ends for the application of an external voltage. It is a two terminal device.




There are two ways of biasing (applying external voltage) a diode.

1. Forward Biasing
2. Reverse Biasing
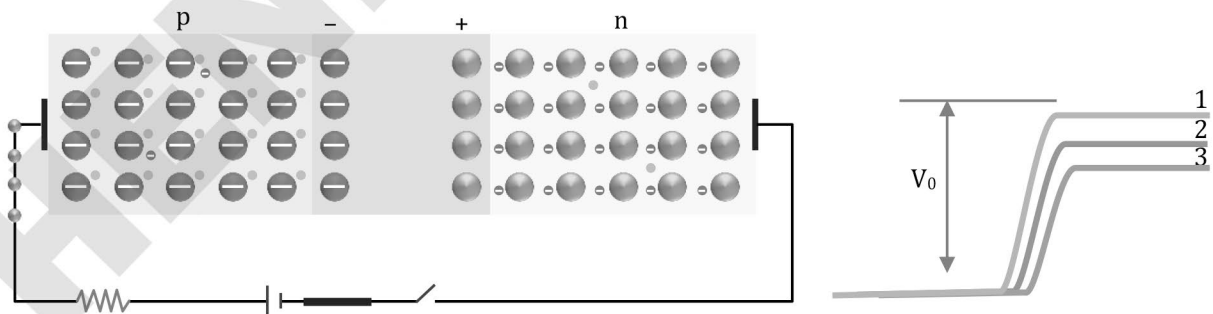
#### 1. Forward Biasing

p-side of semiconductor is connected to the positive terminal of the battery and n-side to the negative terminal. The direction of the applied voltage ( $V$ ) is opposite to the barrier potential  $V_0$ . The depletion layer width decreases and the barrier height is reduced. The effective barrier height under forward bias is  $(V_0 - V)$ .




Current is mainly due to diffusion of charge carriers and it is of the order of mA.

$$|I_{\text{Diffusion}}| > |I_{\text{Drift}}|$$

Forward bias resistance of diode is small and of the order of  $k\Omega$ .

Current is almost zero up to certain value of applied voltage. This voltage is called as knee-Voltage or threshold voltage ( $V_{\text{TH}}$ ).

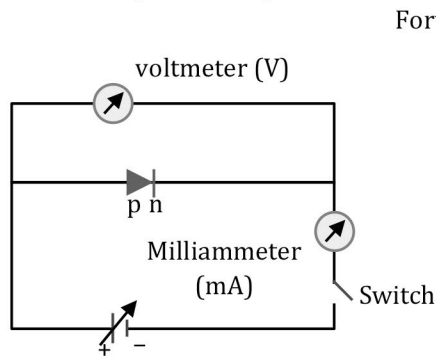
Current increase exponentially after the knee-voltage.



Forward current

( $I_F$  mA)

"Knee voltage"

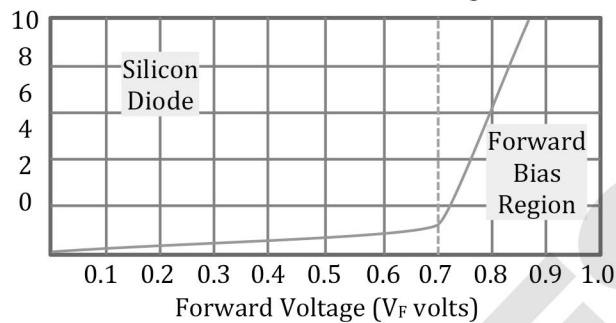

## 2. Reverse Biasing



p-side of semiconductor is connected to the negative terminal of the battery and n-side to the positive terminal. The direction of the applied voltage ( $V$ ) is in support to the barrier potential  $V_0$ . The depletion layer width increases and the barrier height also increases. The effective barrier height under forward bias is  $(V_0 + V)$ . Diffusion of majority carrier stops and current is mainly due to minority carriers. It is of the order of  $\mu\text{A}$ .

$$|I_{\text{Diffusion}}| < |I_{\text{Drift}}|$$




Reverse bias resistance of diode is large and of the order of  $M\Omega$ .

Current is very small & almost constant for any value of applied voltage, as it is limited by the concentration of minority carriers. It is called reverse saturation current ( $I_0$ ).

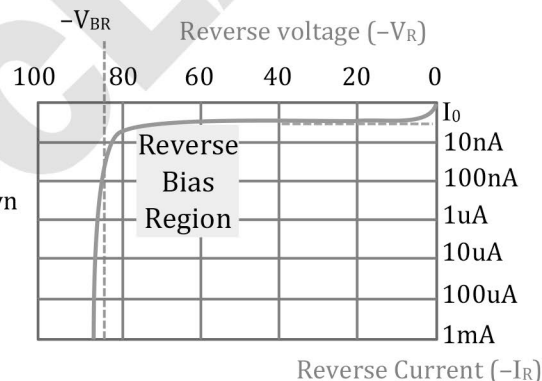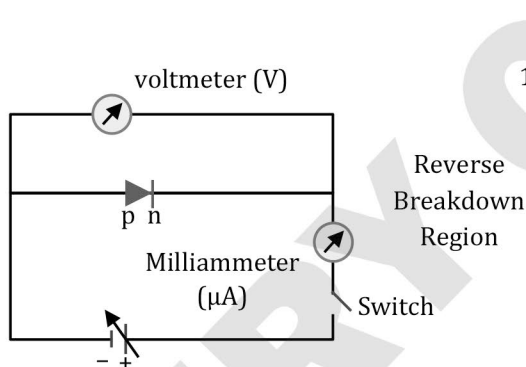When  $V = V_{BR}$ , the diode reverse current increases sharply. Even a slight increase in the bias voltage causes large change in the current.


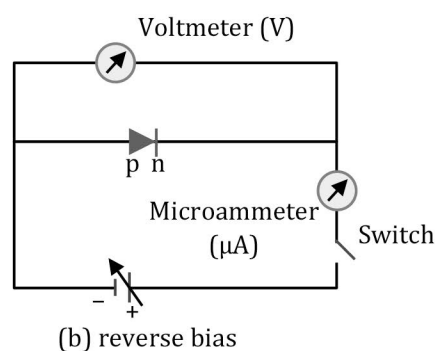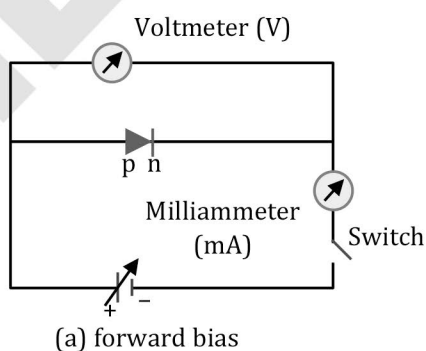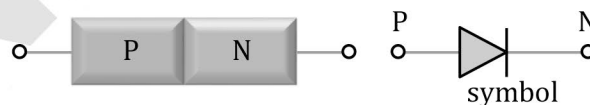
## Characteristic Curve of P-N Junction Diode





In forward bias when voltage is increased from 0V in steps and corresponding value of current is measured, the curve comes as OB of figure. We may note that current increases very sharply after a certain voltage knee voltage. At this voltage, barrier potential is completely eliminated and diode offers a low resistance. In reverse bias a microammeter has been used as current is very small. When reverse voltage is increased from 0V and corresponding values of current measured the plot comes as OCD. We may note that reverse current is almost constant hence called reverse saturation current. It implies that diode resistance is very high. As reverse voltage reaches value  $V_B$ , called breakdown voltage, current increases very sharply.

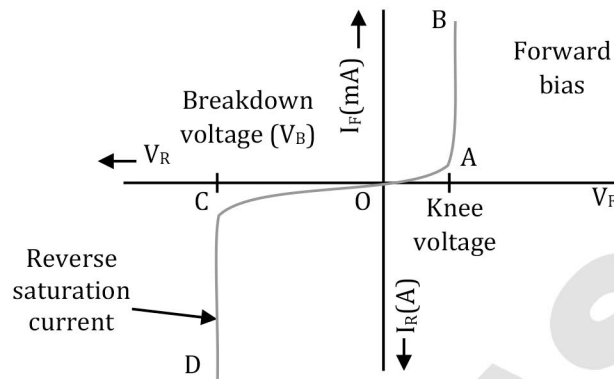
**Illustration 2:**

Figure shows a diode connected to an external resistance and an e.m.f. Assuming that the barrier potential developed in diode is 0.5 V, obtain the value of current in the circuit in milliamperes.


**Solution:**

$$E = 4.5 \text{ V}, R = 100 \Omega,$$

$$\text{Voltage drop across p-n junction} = 0.5 \text{ V}$$

$$\text{Effective voltage in the circuit } V = 4.5 - 0.5 = 4.0 \text{ V}$$


$$\text{Current in the circuit } I = \frac{V}{R} = \frac{4.0}{100} = 0.04 \text{ A} = 0.04 \times 1000 \text{ mA} = 40 \text{ mA}$$

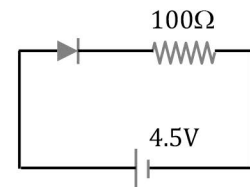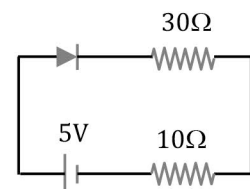**Illustration 3:**

If current in given circuit is 0.1 A then calculate resistance of P-N junction.

**Solution:**


$$\text{Let resistance of PN junction be } R \text{ then } I = \frac{5}{R + 30 + 10} = 0.1 \Rightarrow R = 10 \Omega$$

**Illustration 4:**

What is the value of current I in given circuits?

**Solution:**


$$I = \frac{20}{10 + 10} = 1 \text{ A}$$

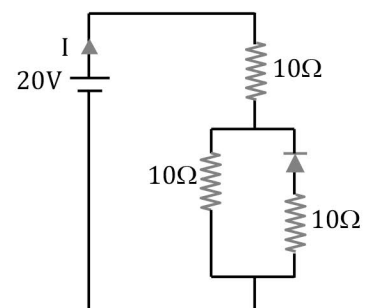



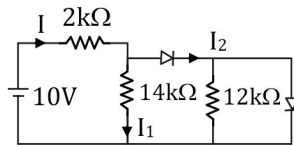
## BEGINNER'S BOX-2


- The potential barrier existing across an unbiased p-n junction is 0.2 volt. What minimum kinetic energy a hole should have to diffuse from the p-side to the n-side if -
  - The junction is unbiased
  - The junction is forward biased at 0.1 volt
  - The junction is reverse-biased at 0.1 volt.
- A silicon P-N junction is in forward biased condition with a resistance in series. It has knee voltage of 0.75 V and current flow in it is 10 mA. If the P-N junction is connected with 2.75 V battery then calculate the value of the resistance.
- In given circuit determine  $I$ ,  $I_1$  and  $I_2$



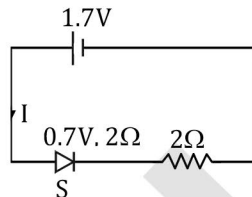- Find the value of current  $I$  in given circuit.



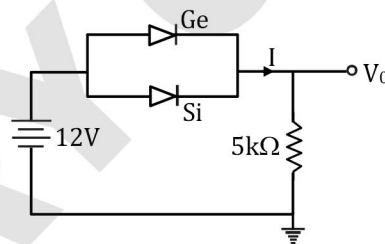- Calculate the value of  $V_0$  and  $I$  if the Si diode and the Ge diode start conducting at 0.7 V and 0.3 V respectively, in the given circuit. (b) If the Ge diode connection be reversed, What will be the new values of  $V_0$  and  $I$ ?





## Application of Junction Diode

### 1. Rectifier

It is device which is used for converting alternating current into direct current. Diode can be used as rectifier as it is uni-directional device.

#### (i) Half Wave Rectifier

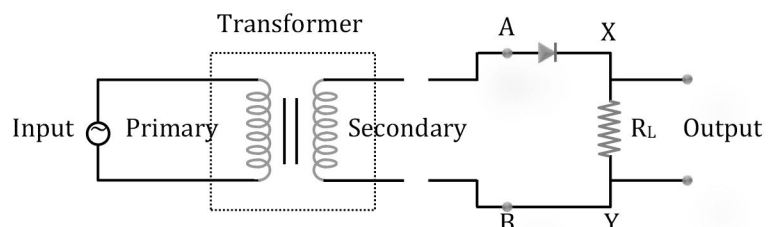


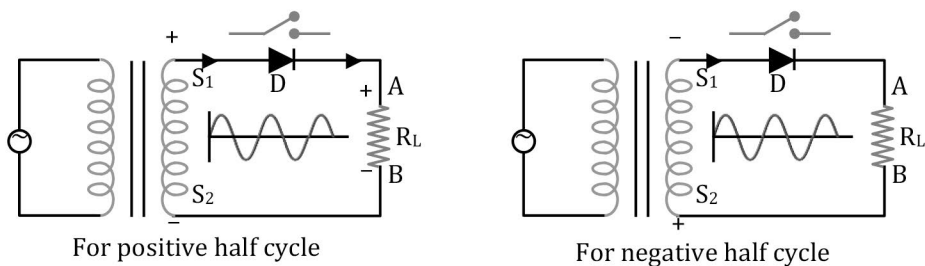**Working:**


During the first half (positive) of the input signal,  $S_1$  is at positive and  $S_2$  is at negative potential. So, the PN junction diode  $D$  is forward biased. The current flows through the load resistance  $R_L$  and output voltage is obtained across the  $R_L$ .

During the second half (negative) of the input signal,  $S_1$  is at negative potential and  $S_2$  is at positive potential. The PN junction diode will be reversed biased. In this case, practically no current would flow through the load resistance. So, there will be no output across the  $R_L$ .

Thus, corresponding to an alternating input signal, we get a unidirectional pulsating output called rectified output.

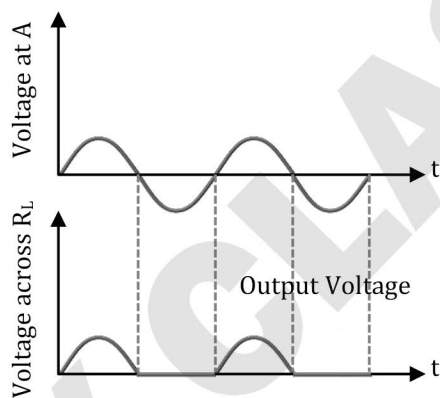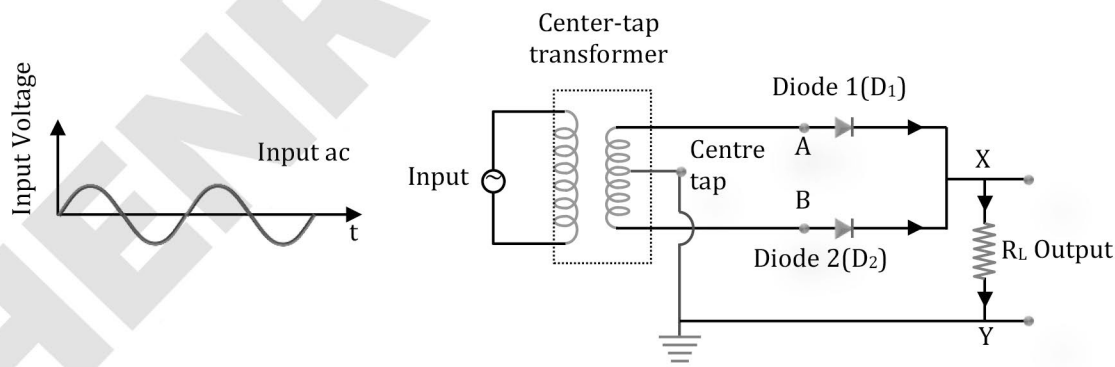**(ii) Full-wave Rectifier (Centre Tap Full Wave Rectifier)**


We need two diodes working for both the half cycles. Also, we need a centre-tap arrangement for transformer.



During the positive half of the input signal :  $S_1$  positive and  $S_2$  negative. In this case diode  $D_1$  is forward biased and  $D_2$  is reverse biased. So only  $D_1$  conducts and hence the flow of current in the load resistance  $R_L$  is from  $A$  to  $B$ .


During the negative half of the input signal :  $S_1$  is negative and  $S_2$  is positive. So  $D_1$  is reverse-biased and  $D_2$  is forward biased. So only  $D_2$  conducts and hence the current flows through the load resistance  $R_L$  again from  $A$  to  $B$ .

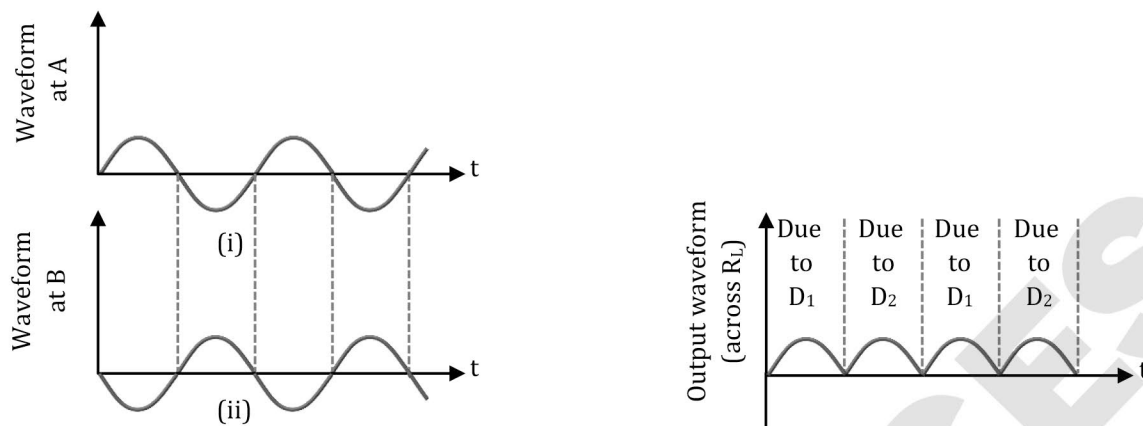It is clear that whether the input signal is positive or negative, the current always flows through the load resistance in the same direction and thus output is called full wave rectified.


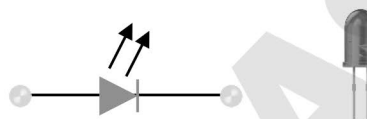
## 2. Light Emitting Diode (L.E.D)

A Light Emitting Diode converts electrical current into light. LEDs are heavily doped p-n junctions and operated under forward bias. Outer material must be transparent so that photons can escape.



**Working :** when LED is forward biased then electrons move from  $N \rightarrow P$  and holes move from  $P \rightarrow N$ . At the junction boundary these are recombined. On recombination, energy is released in the form of photons of energy equal to or slightly less than the band gap.

When the forward current of the diode is small, the intensity of light emitted is small. As the forward current increases, intensity of light increases and reaches a maximum. Further increase in the forward current results in decrease of light intensity. LEDs are biased in such a way that the light emitting efficiency should be maximum.



In case of Si or Ge diodes, the energy released in recombination lies in infra-red region. Therefore to form LED, such semiconductors are to be used which have band gap from 1.8 eV to 3 eV. Hence  $GaAs_{1-x}P_x$  is used in forming LED.

### Advantages of LED:


1. Low operational voltage and less power
2. Fast action with no warm up time
3. Emitted light is nearly monochromatic
4. They have long life
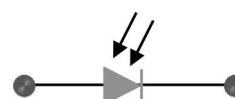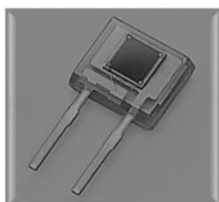
## 3. Photodiode


A photo-diode converts light into electrical current or voltage. Photo-diode are moderately doped p-n junctions and operated under reverse bias. Outer material must be transparent so that photons can enter.



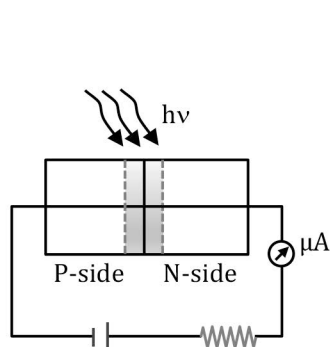**Working:** When light of energy " $h\nu$ " falls on the photodiode (Here,  $h\nu >$  energy gap) more electrons move from valence band to conduction band, due to this current in circuit of photodiode in "Reverse bias", increases. As light intensity is increased, the photo current goes on increasing. So, photo diode is used "to detect light intensity". Example used in "Video camera".



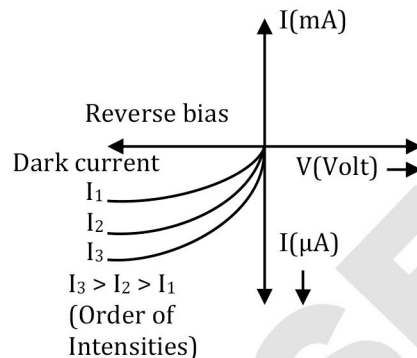
(a) An illuminated photodiode, under reverse bias




(b) I-V characteristics of a photodiode for different illumination intensity  $I_3 > I_2 > I_1$
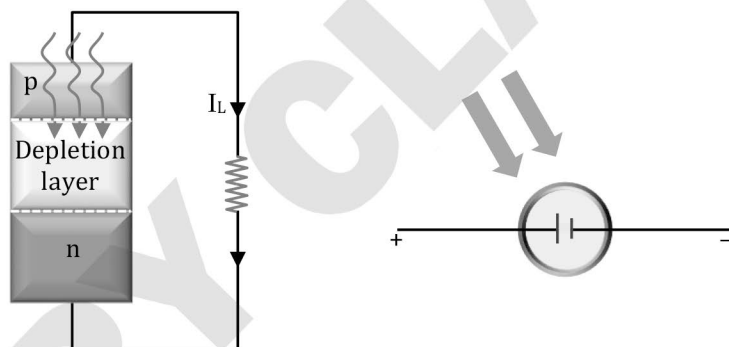
#### 4. Solar Cell

It converts light energy into electrical energy. It has same working principle as that of photo-diode but working method is different. It is operated unbiased. The surface layer of p-region is made very thin so that the incident photons may easily penetrate to reach the junction which is the active region.




**Working:** When light falls on, emf generates due to the following three basic processes: generation, separation and collection- (i) generation of e-h pairs due to light (with,  $h\nu > E_g$ ) in junction region; (ii) separation of electrons and holes due to electric field of the depletion region. Electrons are swept to n-side and holes to p-side by the junction field; (iii) On reaching electrons at n-side and holes on at p-side. Thus n-side becomes negative and p-side becomes positive potential and giving rise to photovoltage.

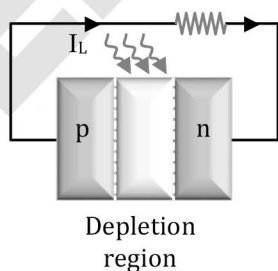

A typical illuminated p-n junction solar cell

(a)

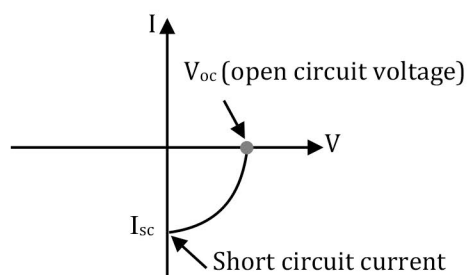


I-V characteristics of a solar cell

(b)

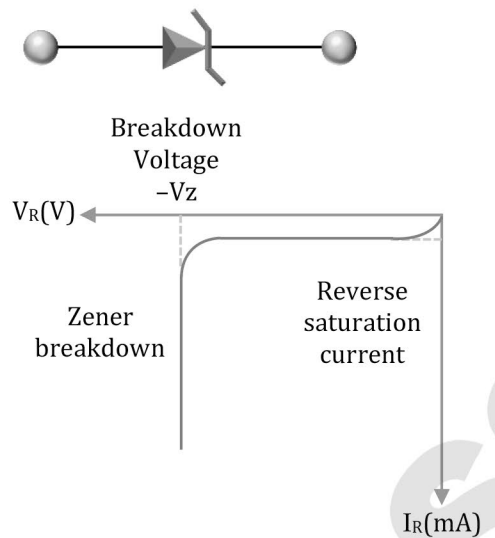
## 5. Zener Diode

Special purpose diode invented by C. Zener. Heavily doped p-n junction. Works like a normal diode in forward bias. Mainly operated in reverse bias breakdown region.



I-V characteristic:

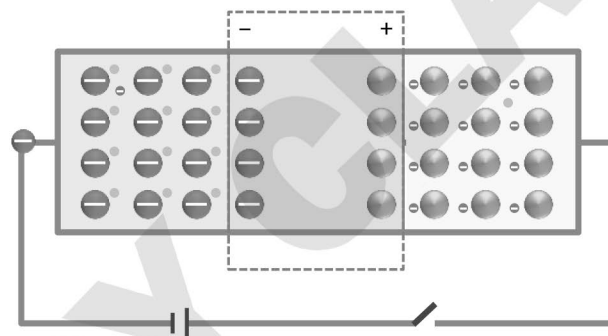It can handle large variation in current without change in Zener voltage, and hence it will be used in regulation.



Increase in reverse bias voltage, increases the  $\vec{E}$  in depletion region.

The electric field may become large enough causing electron-hole pairs to be created.

This creates a huge reverse bias current.

Voltage at which this phenomenon happens is called Breakdown voltage and breakdown voltage is a function of doping concentration in p-region and n-region.

**In reverse biasing, breakdown can occur in two ways:**

1. Avalanche Breakdown
2. Zener Breakdown

### 1. Avalanche Breakdown


It occurs in p-n junction having low doping. Breakdown voltage is very high. Depletion layer width is also more. Charge carriers crossing the depletion region gain enough kinetic energy and make collision with other atoms, and hence it starts the avalanche effect. Damage to the diode is permanent.

### 2. Zener Breakdown


Occurs in heavily doped p-n junction. Breakdown voltage is very small. Depletion layer is very thin. Breaking of covalent bonds is mainly due to electric field. Hence damage is not permanent.
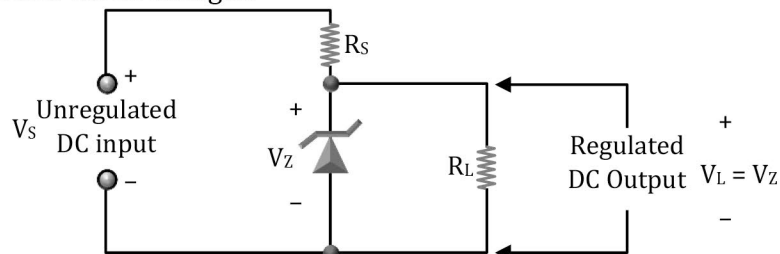
### Zener diode as a voltage regulator

Regulation is possible because in the breakdown region, Zener voltage remains constant even though the current through the Zener diode changes.



If the input voltage increases, the current through  $R_s$  and Zener diode also increases. Similarly, if the input voltage decreases, the current through  $R_s$  and Zener diode also decreases. Thus any increase/decrease in the input voltage results in increase/decrease of the voltage drop across  $R_s$  without any change in voltage across the load. This is how Zener diode acts as a voltage regulator.

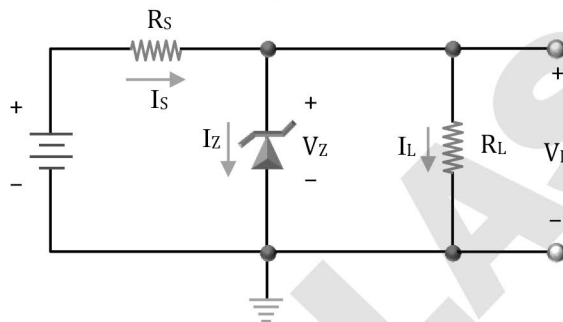



Load voltage is constant and load current is also constant  $\frac{V_Z}{R_L}$ .

Input current is,  $I_s = \frac{V_s - V_Z}{R_s}$ ; Zener Current  $I_Z = I_s - I_L$  and  $P_Z = V_Z I_Z$



### BEGINNER'S BOX-3

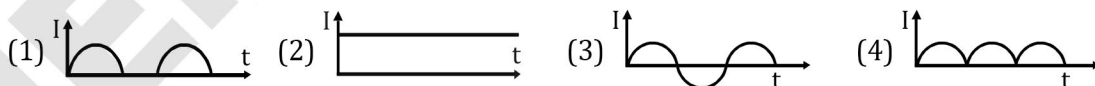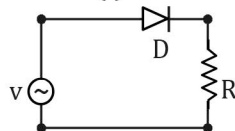1. A p-n junction diode (D) shown in the figure can act as a rectifier. An alternating current source (V) is connected in the circuit. The current (I) in the resistor (R) can be shown by :- [AIEEE - 2009]



2. A zener diode of voltage  $V_Z (=6 \text{ V})$  is used to maintain a constant voltage across a load resistance  $R_L (=1000 \Omega)$  by using a series resistance  $R_s (=100 \Omega)$ . If the e.m.f. of source is  $E (=9 \text{ V})$ , calculate the value of current through series resistance, Zener diode and load resistance. What is the power being dissipated in Zener diode?
3. A Zener diode is specified having a breakdown voltage of  $9.1 \text{ V}$  with a maximum power dissipation of  $364 \text{ mW}$ . What is the maximum current that the diode can handle?
4. A semiconductor (GaAs) has an energy gap of  $1.43 \text{ eV}$ . What is the maximum wavelength emitted when a hole and an electron recombine in such semiconductor?

## Transistor

A transistor is a three terminal electronic device made up of semiconductor material. It is a lot more complex than diode, but with complexity the number of applications increases.

Transistors have many uses, such as: Amplification, Switch, Voltage regulation, Modulation of signals.


Before transistors were invented, circuits used vacuum tubes. Fragile, large in size, heavy, generate large quantities of heat, require a large amount of power. The first transistors were created at Bell Telephone Laboratories in 1947. William Shockley, John Bardeen, and Walter Brattain created the transistors. The word “transistor” is a combination of the terms “transconductance” and “variable resistor”. Today an advanced microprocessor can have as many as 1.7 billion transistors. Transistor and diodes are the main building blocks of all electronic circuits.

### Transistor are of two types


(a) NPN transistor

(b) PNP transistor

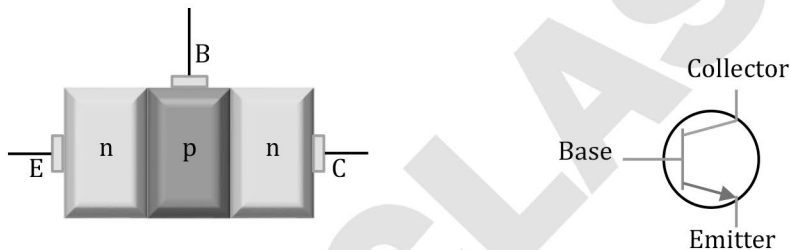**(a) NPN transistor:** If a thin layer of P-type semiconductor is sandwiched between two thick layers of N-type semiconductor, then it is known as NPN transistor.



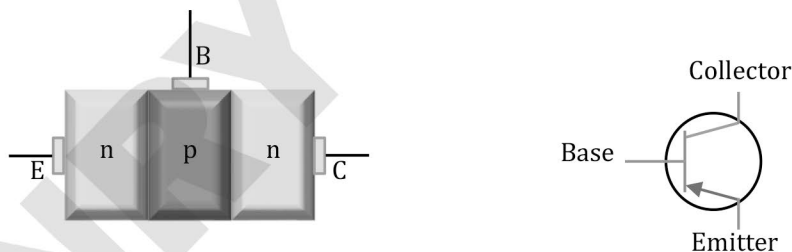**(b) PNP transistor :** If a thin layer of N-type of semiconductor is sandwiched between two thick layer of P-type semiconductor, then it is known as PNP transistor.



### Each transistor has three terminals

**Emitter:** It is moderate size and heavily doped. It supplies a large number of majority carriers for the current flow through the transistor.

**Base:** It is very thin & lightly doped as we want very less recombination of charge carriers.

**Collector:** It is moderately doped and larger in size as compared to the emitter. Larger size helps in proper heat dissipation.

↓   ⇒	Emitter	Base	Collector
Sizes	Moderate	Thin	Large
Doping Level	Heavy	Light	Moderate



**Transistor has two p-n junctions:**


- (a) Base-Emitter (b) Base-Collector

Based on the biasing of these junctions, its region of operation and application will be different

Base-Emitter	Base-Collector	Region	Application
Forward	Reverse	Active	Amplification
Forward	Forward	Saturation	Switch "ON"
Reverse	Reverse	Cut-Off	Switch "OFF"
Reverse	Forward	Inverse-Active	--NA--

**Working of Transistor****1. Working of NPN Transistor**

The emitter base junction is forward biased and base collector junction is reversed biased to study the behaviour of transistor. It is called active state of transistor. N-P-N transistor in circuit and symbolic representation is shown in figure.

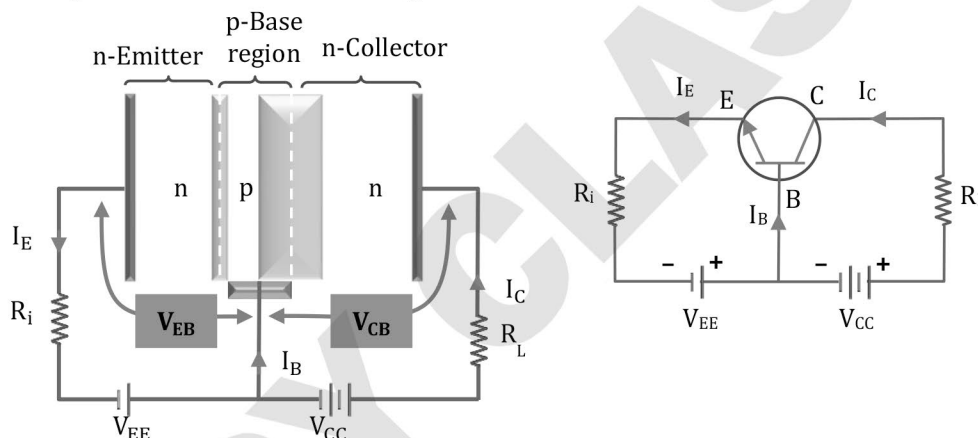**Common Base NPN Transistor**

In active state of n-p-n transistor majority electrons in emitter are sent towards base.

The barrier of emitter base junction is reduced because of forward bias therefore electrons enter into the base. About 5% of these electrons recombine with holes in base region results very small current ( $I_B$ ) in base.


The remaining electron (95%) enters into the collector region because these are attracted towards the positive terminal of battery results collector current ( $I_C$ )

The base current is the difference between  $I_E$  and  $I_C$  and proportional to the number of electron hole recombination in the base.

$I_E = I_B + I_C$ , We also see  $I_E = I_C$ ; because  $I_B$  is very small.

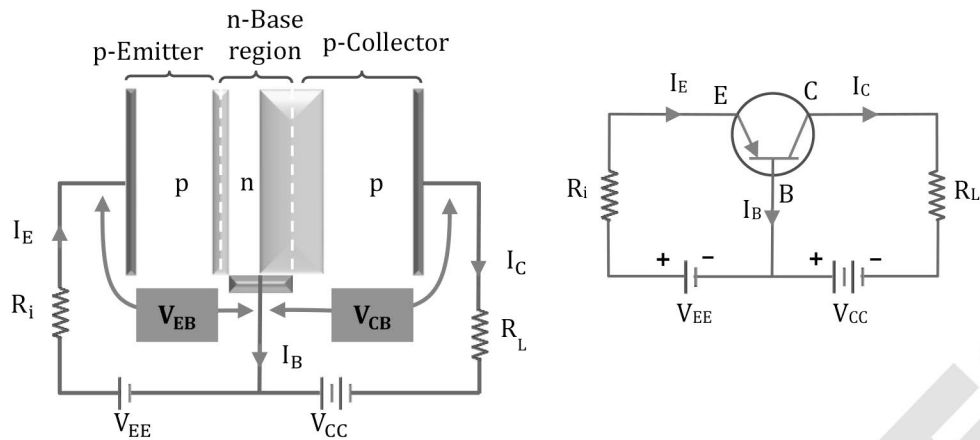**2. Working of PNP Transistor**

When emitter-base junction is forward biased, holes (majority carriers) in the emitter are repelled towards the base and diffuse through the emitter base junction. The barrier potential of emitter-base junction decreases and hole enters into the n-region (i.e. base). A small number of holes (5%) combine with electrons of base-region resulting small current ( $I_B$ ). The remaining holes (95%) enter into the collector region because these are attracted towards negative terminal of the battery connected with the collector-base junction. These holes constitute the collector current ( $I_C$ ).




### Common Base PNP Transistor

As one hole reaches the collector, it is neutralized by the battery. As soon as one electron and a hole is neutralized in collector, a covalent bond is broken in emitter region and an electron hole pair is produced. The released electron enters the positive terminal of battery and holes moves towards the collector. So,  $I_E = I_B + I_C$

### Configuration of Transistor


The transistor is connected in either of the three ways in circuit.

(i) Common base configuration

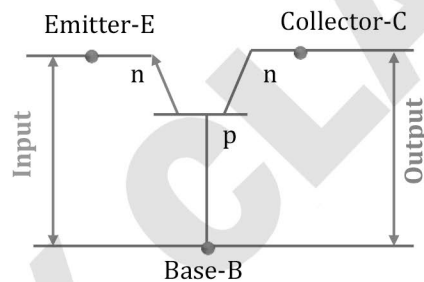


Common Base (CB) configuration

(ii) Common emitter configuration

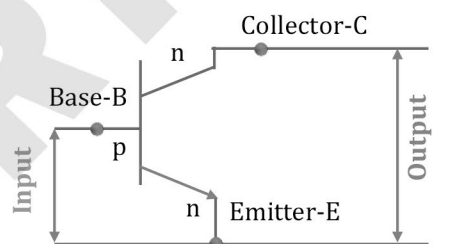

Common Emitter (CE) configuration

(iii) Common collector configuration

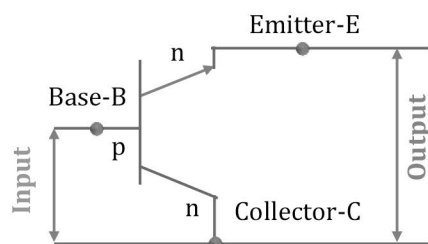


Common collector (CC) configuration

In these three, common emitter is widely used and common collector is rarely used.
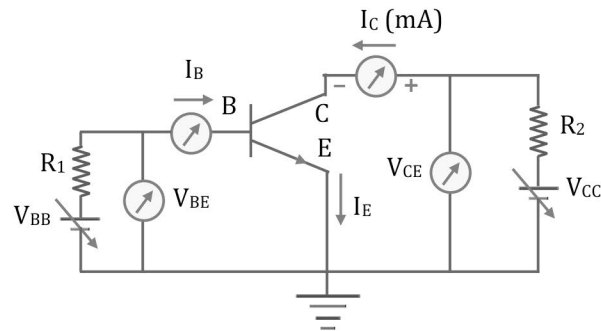
### Common emitter configuration

Input signal is provided between the emitter and the base. Output signal appears across the collector and the emitter.



The configuration in which the emitter is connected between the collector and base is known as a common emitter configuration. The variation of base current ( $I_B$ ) with Base-Emitter voltage ( $V_{BE}$ ), keeping Collector Emitter voltage ( $V_{CE}$ ) constant.

The current gain ( $\beta_{DC}$ ) in CE mode of a transistor is given by,  $\beta_{DC} = \frac{I_C}{I_B}$



The current gain ( $\beta_{AC}$ ) in CE mode of a transistor is given by,  $\beta_{AC} = \left( \frac{\Delta I_C}{\Delta I_B} \right)_{V_{CE}=\text{constant}}$

$\beta$  is in the range of about 50 to 300.

### Transistor characteristics
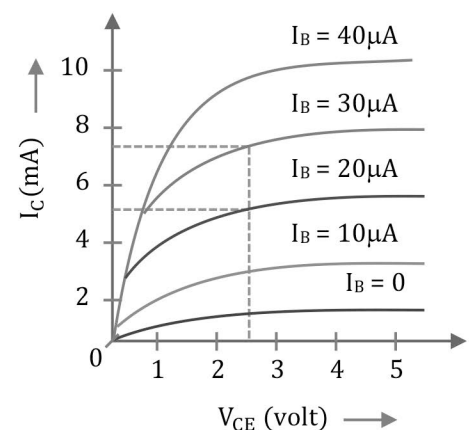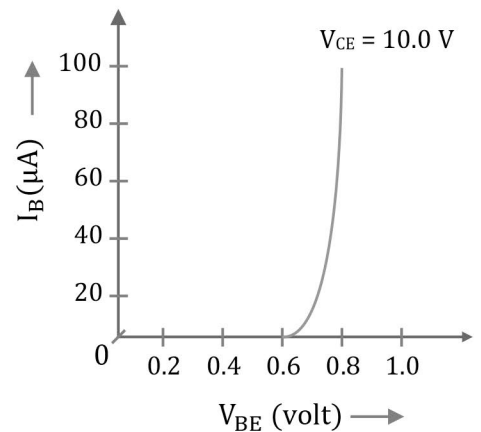
#### Common emitter transistor characteristics

- Input characteristics:** The variation of base current ( $I_B$ ) (input) with base emitter voltage ( $V_{EB}$ ) at constant collector emitter voltage ( $V_{CE}$ ) is called input characteristic.
  - Keep the collector-emitter voltage ( $V_{CE}$ ) constant (say  $V_{CE} = 10 \text{ V}$ )
  - Now change emitter base voltage  $V_{BE}$  in steps of 0.1 volt and note the corresponding values of base current ( $I_B$ ).
  - Plot the graph between  $V_{BE}$  and  $I_B$ .
- Output characteristics:** The variation of collector current  $I_C$  (output) with collector-emitter voltage ( $V_{CE}$ ) at constant base current ( $I_B$ ) is called output characteristic.
  - Keep the base current ( $I_B$ ) constant (say  $I_B = 10 \mu\text{A}$ )
  - Now change the collector-emitter voltage ( $V_{CE}$ ) and note the corresponding values of collector current ( $I_C$ ).
  - Plot the graph between  $V_{CE}$  and  $I_C$ .
  - A set of such curves can also be plotted at different fixed values of base current (say  $20 \mu\text{A}$ ,  $30 \mu\text{A}$  etc.)



Relation Between  $\alpha$ ,  $\beta$  and  $\gamma$ 

$\alpha, \beta$	$\beta, \gamma$	$\alpha, \gamma$
$I_E = I_B + I_C$ ; divide by $I_C$	$I_E = I_B + I_C$ ; divide by $I_B$	$I_E = I_B + I_C$
$\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$	$\frac{I_E}{I_B} = 1 + \frac{I_C}{I_B}$	$\therefore \gamma = 1 + \beta$ $\gamma = 1 + \frac{\alpha}{1-\alpha}$
$\frac{1}{\alpha} = \frac{1}{\beta} + 1$	$\gamma = 1 + \beta$	$\gamma = \frac{1}{1-\alpha}$
$\beta = \frac{\alpha}{1-\alpha}, \alpha = \frac{\beta}{1+\beta}$		$\alpha \cdot \gamma = \beta$

**Illustration 5:**

In a transistor, the value of  $\beta$  is 50. Calculate the value of  $\alpha$ .

**Solution:**

$$\beta = \frac{\alpha}{1-\alpha} \Rightarrow 50 = \frac{\alpha}{1-\alpha} \Rightarrow 50 - 50\alpha = \alpha \Rightarrow \alpha = \frac{50}{51} = 0.98$$

**Illustration 6:**

Calculate the emitter current for which  $I_B = 20 \mu\text{A}$ ,  $\beta = 100$ .

**Solution:**

$$I_C = \beta \times I_B = 100 \times 20 \times 10^{-6} = 2000 \mu\text{A}$$

$$I_E = I_B + I_C = 20 + 2000 = 2020 \mu\text{A} = 2.02 \times 10^{-3} \text{ A} = 2.02 \text{ mA}$$

**Illustration 7:**

The base current is  $100 \mu\text{A}$  and collector current is  $3 \text{ mA}$ .

- (a) Calculate the values of  $\beta$ ,  $I_E$  and  $\alpha$
- (b) A change of  $20 \mu\text{A}$  in the base current produces a change of  $0.5 \text{ mA}$  in the collector current. Calculate  $\beta_{ac}$ .

**Solution:**

$$(a) \quad \beta = \frac{I_C}{I_B} = \frac{3 \times 10^{-3}}{100 \times 10^{-6}} = 30 \Rightarrow \alpha = \frac{\beta}{1+\beta} = \frac{30}{1+30} = \frac{30}{31} = 0.97 \text{ and } I_E = \frac{I_C}{\alpha} = \frac{3 \times 31}{30} = 3.1 \text{ mA}$$

$$(b) \quad \Delta I_B = 20 \mu\text{A} = 0.02 \text{ mA} \Rightarrow \Delta I_C = 0.5 \text{ mA}$$

$$\therefore \beta_{ac} = \frac{\Delta I_C}{\Delta I_B} = \frac{0.5}{0.02} = 25$$

**Illustration 8:**


In a transistor connected in common emitter mode  $R_0 = 4 \text{ k}\Omega$ ,  $R_i = 1 \text{ k}\Omega$ ,  $I_C = 1 \text{ mA}$  and  $I_B = 20 \mu\text{A}$ . Find the voltage gain.

**Solution:**

$$\text{Voltage gain, } A_V = \beta \left( \frac{R_0}{R_i} \right) = \left( \frac{I_C}{I_B} \right) \left( \frac{R_0}{R_i} \right) = \left( \frac{1 \times 10^{-3}}{20 \times 10^{-6}} \right) \left( \frac{4}{1} \right) = 200$$

**Illustration 9:**

For given CE biasing circuit, if voltage across collector-emitter is 12 V and current gain is 100 and base current is 0.04 mA then determine the value of collector resistance  $R_C$ .

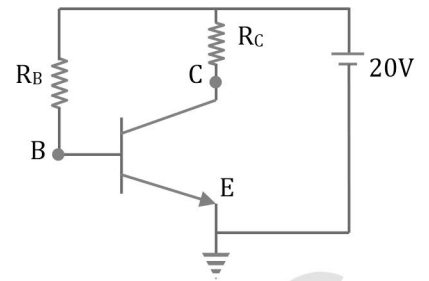**Solution:**

$$\therefore V_{CE} = V_{CC} - I_C \times R_C$$

$$\therefore R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{V_{CC} - V_{CE}}{\beta I_B} = \frac{20 - 12}{100 \times 0.04 \times 10^{-3}} = 2 \text{ k}\Omega$$

**Illustration 10:**

Two amplifiers are connected one after the other in series (cascaded). The first amplifier has a voltage gain of 10 and the second has a voltage gain of 20. If the input signal is 0.01 volt, calculate the output signal.

**Solution:**

$$\therefore A = A_1 \times A_2 = 10 \times 20 = 200$$

$$\therefore \text{Output signal} = A \times \text{input signal} = 200 \times 0.01 = 2 \text{ V}$$


**Comparison between Common Base, Common Collector, Common Emitter**

Comparison factors	Common Base (CB)	Common Emitter (CE)	Common Collector (CC)
Circuit Diagram			
Input Resistance	Low (100 $\Omega$ )	High (750 $\Omega$ )	Very High $\cong 750 \text{ k}\Omega$
Output resistance	Very High	High	Low
Current Gain	( $A_I$ or $\alpha$ ) $\alpha = \frac{I_C}{I_E} < 1$	( $A_I$ or $\beta$ ) $\beta = \frac{I_C}{I_B} > 1$	( $A_I$ or $\gamma$ ) $\gamma = \frac{I_E}{I_B} > 1$
Voltage Gain	$A_V = \frac{V_o}{V_i} = \frac{I_C R_L}{I_E R_i}$ $A_V = \alpha \frac{R_L}{R_i}$	$A_V = \frac{V_o}{V_i} = \frac{I_C R_L}{I_B R_i}$ $A_V = \beta \frac{R_L}{R_i}$	$A_V = \frac{V_o}{V_i} = \frac{I_E R_L}{I_B R_i}$ $A_V = \gamma \frac{R_L}{R_i}$
Power Gain	$A_p = \frac{P_o}{P_i}$ $A_p = \alpha^2 \frac{R_L}{R_i}$	$A_p = \frac{P_o}{P_i}$ $A_p = \beta^2 \frac{R_L}{R_i}$	$A_p = \frac{P_o}{P_i}$ $A_p = \gamma^2 \frac{R_L}{R_i}$
Phase difference (between output and input)	Same phase	Opposite phase	Same phase
Application	For High Frequency amplifier	For Audible frequency amplifier	For Impedance Matching

## Applications of Transistor
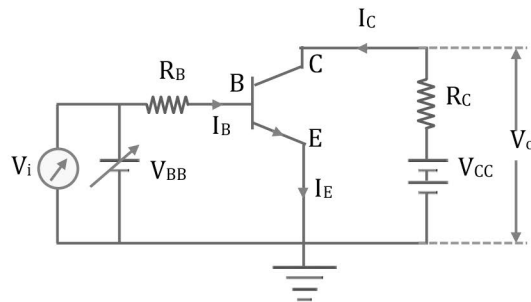
### 1. Transistor as switch

When a transistor is used in the cut off (off state) or saturation state (on state) only, it acts as a switch. To study this behaviour, we understand base biased CE transistor circuit.




Applying Kirchoff's voltage rule to the input and output sides of this circuit we get,

$$V_i = I_B R_B + V_{BE} \quad (V_i = \text{dc input voltage})$$

$$\text{and } V_o = V_{CC} - I_C R_C \quad (V_o = \text{dc output voltage})$$

Now we can analyse how  $V_o$  changes as  $V_i$  increase from zero onwards. In case of Silicon transistor, if  $V_i$  is less than 0.6 V,  $I_B$  will be zero, hence  $I_C$  will be zero and transistor will be said to be in cut-off state, and  $V_o = V_{CC}$ . When  $V_i$  become greater than 0.6 V, some  $I_B$  flows, so some  $I_C$  flows (transistor is in active state now) and output  $V_o$  decreases as the term  $I_C R_C$  increase. With increase in  $V_i$  the  $I_C$  increase almost linearly and so  $V_o$  decreases linearly till its value becomes less than about 1.0 volt.

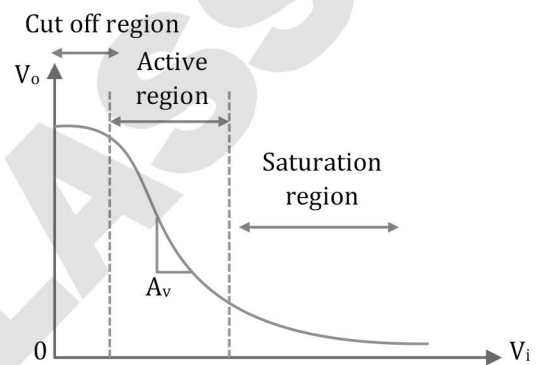


Beyond this, the change becomes non-linear and transistor goes into saturation state. With further increase in  $V_i$  the output voltage is found to decrease further towards zero (however, it may never become zero). If we draw the  $V_o$  versus  $V_i$  curve called transfer characteristic (see figure), we see that between cut off state and active state and also between active state and saturation state there are regions of non-linearity showing that the transition from cut-off state to active state and from active state to saturation state are not sharply defined.
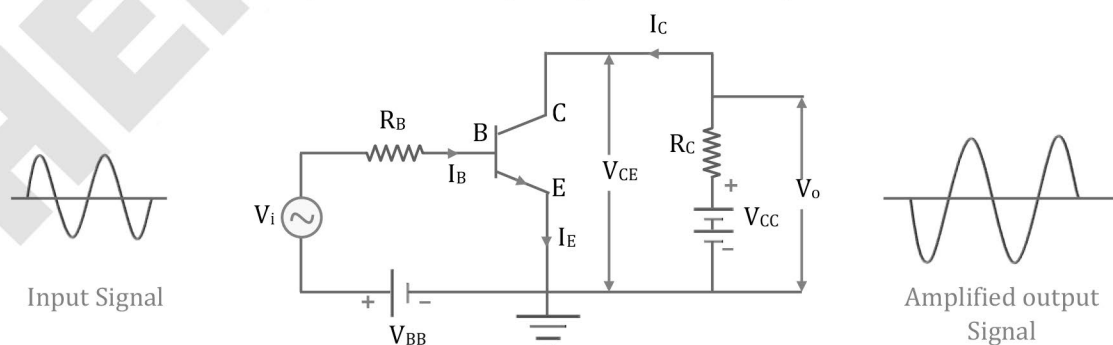
### 2. Transistor as amplifier

The process of increasing the amplitude of input signal without distorting its wave shape and without changing its frequency is known as amplification.

A device which increases the amplitude of the input signal is called amplifier.



Common Emitter Amplifier NPN Transistor

To operate the transistor as an amplifier it is necessary to fix its operating point somewhere in the middle of its active region. If we fix the value of  $V_{BB}$  corresponding to a point in the middle of the linear part of the transfer curve then the dc base current  $I_B$  would be constant and corresponding collector current  $I_C$  will also be constant. The dc voltage,  $V_{CE} = V_{CC} - I_C R_C$  would also remain constant. The operating values of  $V_{CE}$  and  $I_B$  determine the operating point of the amplifier.

If a small sinusoidal voltage with amplitude  $u_i$  is superposed in series with the  $V_{BB}$  supply, then the base current will have sinusoidal variations superimposed on the value of  $I_B$ . As a consequence the collector current also will have sinusoidal variations superimposed on the value of  $I_C$  producing in turn corresponding change in the value of  $V_o$ .

Mathematical Analysis : From KVL equation of base biased CE transistor circuit,

$$V_i = I_B R_B + V_{BE}$$

$$\Rightarrow \Delta V_i = (\Delta I_B) R_B + \Delta V_{BE} \quad (\because \Delta V_{BE} = 0) \quad \Rightarrow \quad \Delta V_i = (\Delta I_B) R_B$$

$$\text{Similarly, } V_o = V_{CC} - I_C R_C$$

$$\Rightarrow \Delta V_o = \Delta V_{CC} - (\Delta I_C) R_C \quad (\because \Delta V_{CC} = 0) \quad \Rightarrow \quad \Delta V_o = -(\Delta I_C) R_C$$

So voltage gain of CE amplifier,

$$A_v = \frac{\Delta V_o}{\Delta V_{in}} = \frac{-(\Delta I_C) R_C}{(\Delta I_B) R_B} = -\beta \frac{R_C}{R_B}$$

The negative sign represents that output voltage is opposite in phase with the input voltage.

Power gain ( $A_p$ ) = current gain  $\times$  voltage gain =  $\beta_{ac} \times A_v$  (always,  $A_p > 1$ )


**Note:** However, it should be realised that transistor is not a power generating device. The energy for the higher ac power at the output is supplied by the battery  $V_{CC}$ .

### 3. Transistor as oscillator

Oscillator is device which delivers ac output wave form of desired frequency without any external input wave form.

The electric oscillations are produced by L - C circuit (i.e. tank circuit containing inductor and capacitor). These oscillations are damped one i.e. their amplitude decrease with the passage of time due to the small resistance of the inductor. In other words, the energy of the L - C oscillations decreases. If this loss of energy is compensated from outside, then undamped oscillations (of constant amplitude) can be obtained. This can be done by using feed back arrangement and a transistor amplifier in the circuit.


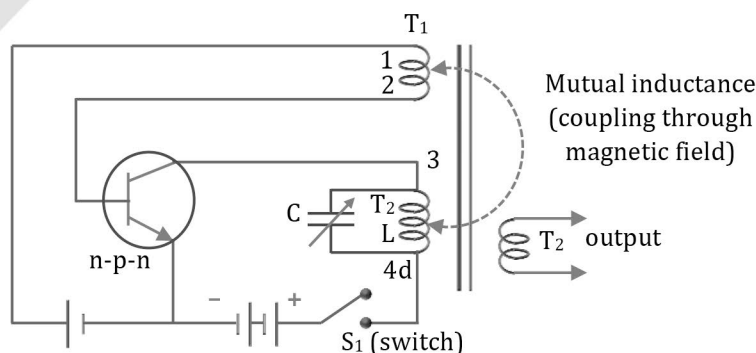
Oscillating frequency of oscillator is given by  $f = \frac{1}{2\pi\sqrt{LC}}$




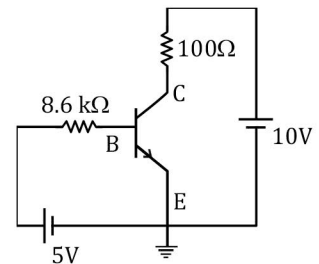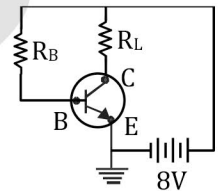
## BEGINNER'S BOX-4

- For a common emitter amplifier, current gain = 50. If the emitter current is 6.6 mA, calculate the collector and base current. Also calculate current gain, when emitter is working as common base amplifier.
- Transistor with  $\beta = 75$  is connected to common-base configuration. What will be the maximum collector current for an emitter current of 5 mA ?
- In npn transistor circuit, the collector current is 10 mA. If 95% of the electrons emitted reach the collector, what is the base current ?
- In an NPN transistor  $10^{10}$  electrons enter the emitter in  $10^{-6}$  s and 2% electrons recombine with holes in base, then current gain  $\alpha$  and  $\beta$  are :
- For a CE amplifier, current gain is 69. If the emitter current is 7 mA then calculate the base current and collector current. **[AIPMT (Mains) 2008]**
- An n-p-n transistor in a common emitter mode is used as a simple voltage amplifier with a collector connected to load resistance  $R_L$  and to the base through a resistance  $R_B$ . The collector-emitter voltage  $V_{CE} = 4$  V, the base-emitter voltage  $V_{BE} = 0.6$  V, Current through collector is 4 mA and the current amplification factor  $\beta = 100$ . Calculate the values of  $R_L$  and  $R_B$ .
- A common emitter amplifier has a voltage gain of 50, an input impedance of  $200 \Omega$  and an output impedance of  $400 \Omega$ . Calculate the power gain of the amplifier.
- A silicon transistor amplifier ckt. is given here. If  $\beta = 100$  then determine
  - Base current  $I_B$
  - Collector current  $I_C$
  - $V_{CE}$
 Take the voltage drop between base and emitter as 0.7 V.



## Boolean Algebra

### Analog v/s Digital Electronics


Analog Signal	Digital Signal
<p>A continuous signal value which at any instant lies within the range of a maximum and a minimum value.</p>	<p>A discontinuous (discrete) signal value which appears in steps in pre-determined levels rather than having the continuous change.</p>
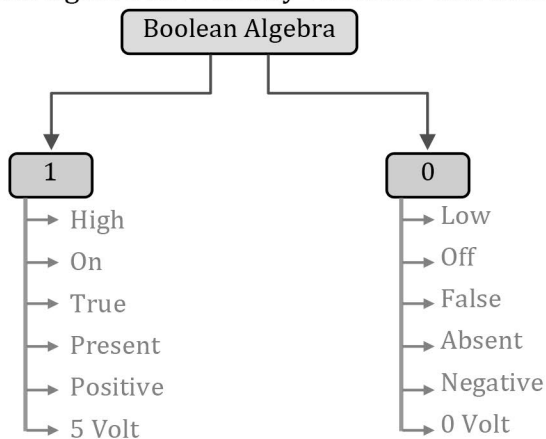
## Digital Circuit

An electrical or electronic circuit which operates only in two states (binary mode) namely ON/1 and OFF/0 is called a Digital Circuit. To understand the Digital circuits, we need to understand the Boolean algebra. Boolean Algebra was invented by George Boole.



Boolean algebra have binary variables that take only 2 discrete values (0 and 1).



OR	AND	NOT
$0+0=0$	$0.0=0$	$0'=\bar{0}=1$
$0+1=1$	$0.1=0$	$1'=\bar{1}=0$
$1+0=1$	$1.0=0$	
$1+1=1$	$1.1=1$	
FORMULAE		
$A+0=A$	$A.0=0$	$A+A'=1$
$A+1=1$	$A.1=A$	$A.A'=0$
$A+A=A$	$A.A=A$	$A''=A$

### Boolean Algebra Laws

#### Commutative law :

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

#### Associative law :

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

#### Distributive law :

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

#### De-Morgan's Theorem:

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

#### Illustration 11:

By using Boolean Algebra prove that,  $\bar{A}B + A\bar{B} + AB = A + B$

#### Solution:

$$\text{LHS} = \bar{A}B + A\bar{B} + AB = \bar{A}B + A\bar{B} + AB + AB = A(B + \bar{B}) + B(\bar{A} + A) = A \cdot 1 + B \cdot 1 = A + B = \text{RHS}$$

### Logic Gates

A logic gate is a digital circuit which is based on certain logical relationship between the input and the output voltages of the circuit.

The logic gates are built using the Semiconductor diodes and transistors.

These are the basic building blocks of a digital circuit.

#### Basic logic gates

##### 1. OR Gate

Representation :





Boolean expression :  $Y = A + B$

Truth table :

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**Note :** Output is ON if any of the inputs are ON.

Electric analogous circuit :

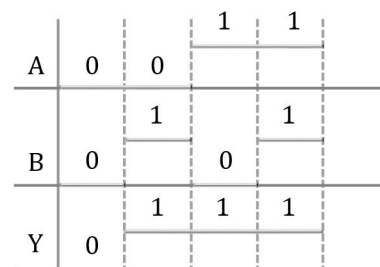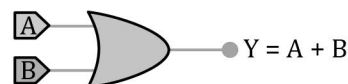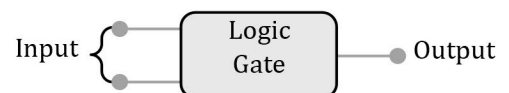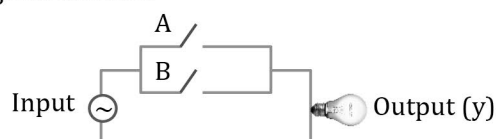

Waveforms



## 2. AND Gate

Representation :

Boolean expression :  $Y = A \cdot B$


Truth table :

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

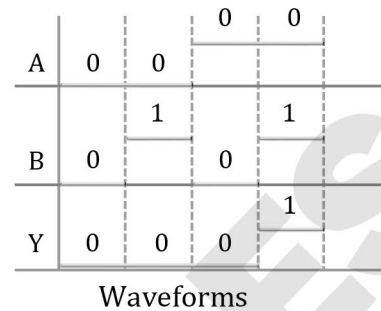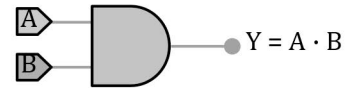

**Note :** Output is ON if and only if all the inputs are ON.

Electric analogous circuit :

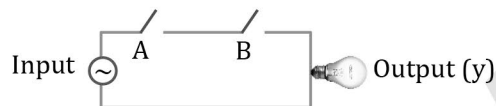



## 3. NOT Gate (Inverter)

Representation :

Boolean expression :  $Y = \bar{A}$

Truth table :

A	Y
0	1
1	0

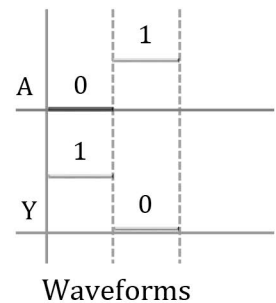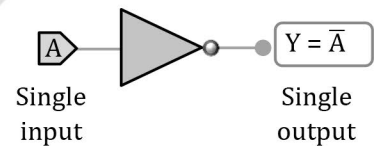

**Note :** The output of a NOT gate attains the state ON if and only if the input does not attain the state ON.


Electric analogous circuit :



## Universal gates

### 1. NAND Gate


Representation :

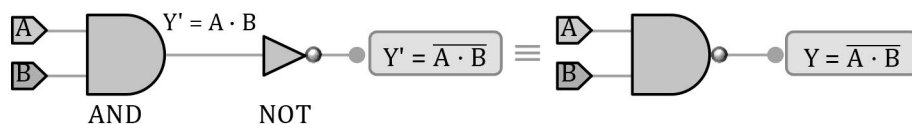

Boolean expression :  $Y = \overline{A \cdot B}$

Truth table :

A	B	$Y' = A \cdot B$	$Y = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

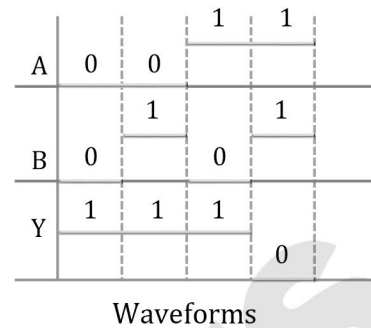


**Note :** The output is low only when both the input are high.

Electric analogous circuit :



## 2. NOR Gate


Representation :

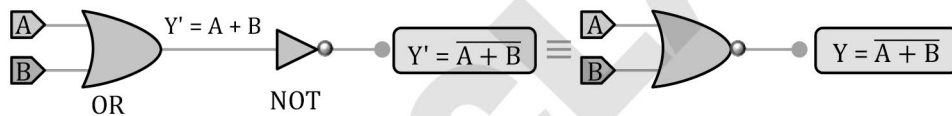

Boolean expression :  $Y = \overline{A + B}$


Truth table :

A	B	$Y' = A + B$	$Y = \overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

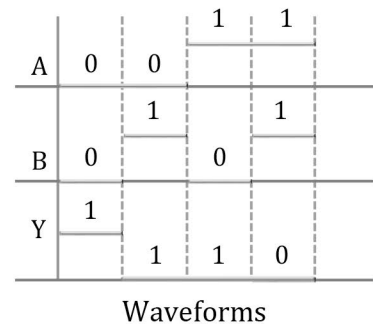

**Note :** The gate give high output only when both the inputs are low.


Electric analogous circuit :

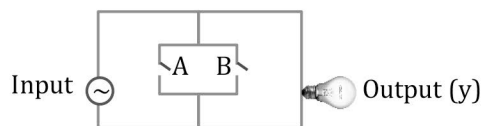

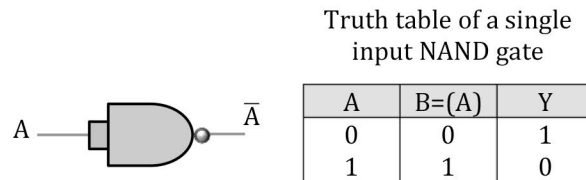
## Realization of gates by universal gates

The NAND or NOR gate is the universal building block of all digital circuits. Repeated use of NAND gates (or NOR gates) gives other gates. Therefore, any digital system can be achieved entirely from NAND or NOR gates. We shall show how the repeated use of NAND (and NOR) gates will gives us different gates.


**The NOT gate from a NAND gate :-** When all the inputs of a NAND gate are connected together, as shown in the figure, we obtain a NOT gate.



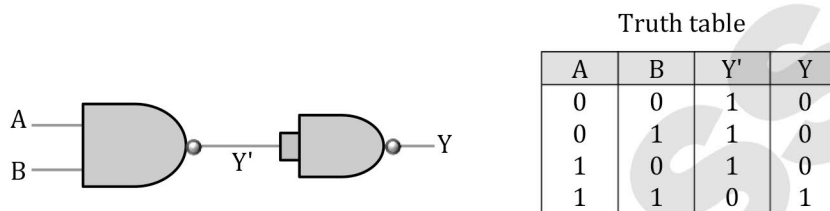
**The AND gate from a NAND gates :-** If a NAND gate is followed by a NOT gate (i.e., a single input NAND gate), the resulting circuit is an AND gate as shown in figure and truth table given show how an AND gate has been obtained from NAND gates.



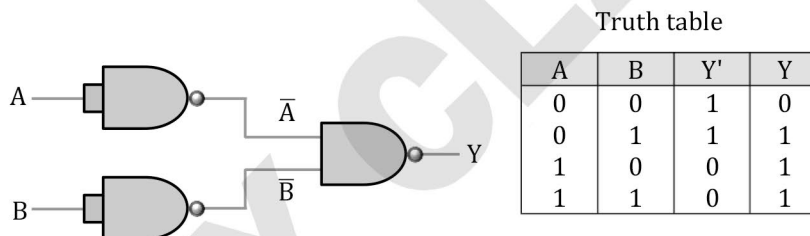
**The OR gate from NAND gates :-** If we invert the inputs A and B and then apply them to the NAND gate, the resulting circuit is an OR gate.



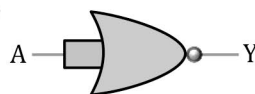
**The NOT gate from NOR gates :-** When all the inputs of a NOR gate are connected together as shown in the figure, we obtain a NOT gate



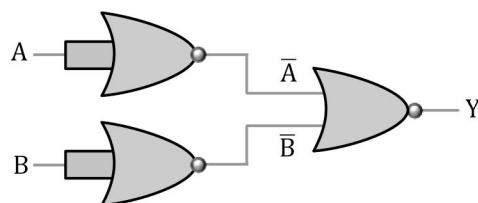**The AND gate from NOR gates :-** If we invert the inputs A and B and then apply them to the NOR gate, the resulting circuit is an AND gate.




**The OR gate from NOR gate :-** If a NOR gate is followed by a single input NOR gate (NOT gate), the resulting circuit is an OR gate.

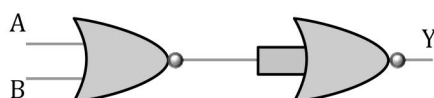

**Illustration 12:**


Write down output Y in terms of inputs A and B.

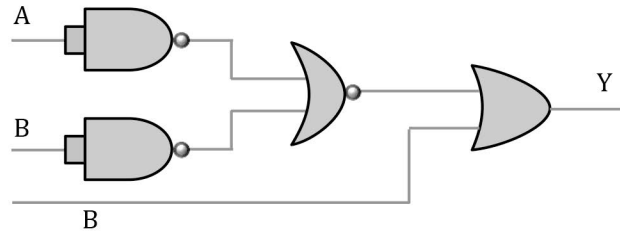**Solution:**

$$Y = \overline{A+B} + B = \overline{A} \cdot \overline{B} + B = A \cdot B + B = (A+1)B = B$$

**Illustration 13:**

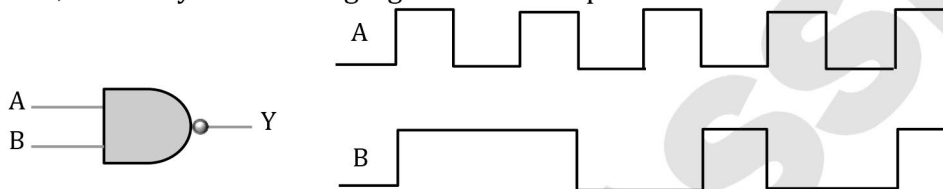In the figures below, Circuit symbol of a logic gate and two input waveforms 'A' and 'B' are shown.



- Name the logic gate & Write its Boolean expression
- Write its truth table
- Give the output wave form

**Solution:**

(a) NAND gate ;


(b) Truth table

Input A	Input B	Output Y
0	0	1
0	1	1
1	0	1
1	1	0


(c) Output waveform

**Illustration 14:**

Given electrical circuit is equivalent to which logic gate, also draw its symbol and truth table.

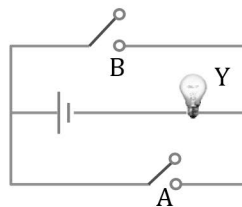**Solution:**

OR gate

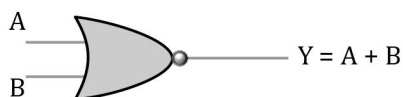

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**Illustration 15:**


Write the truth table for the logical function  $D = (A \text{ AND } B) \text{ OR } B$

**Solution:**

A	B	$X = A \text{ AND } B$	$D = X \text{ OR } B$
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	1

**Illustration 16:**

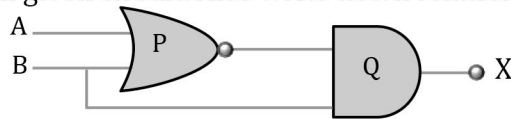Identify the logic gates P and Q in given circuit. Also write down relation in A, B and X.




**Solution:**

P is NOR gate & Q is AND gate,  $X = (\overline{A+B}) \cdot B = (\overline{A} \cdot \overline{B}) \cdot B = \overline{A} \cdot (\overline{B} \cdot B) = \overline{A} \cdot 0 = 0$

**Special purpose gates****1. XOR Gate**


Representation :

Boolean expression :  $Y = \overline{A} \cdot B + A \cdot \overline{B}$  or  $Y = A \oplus B$

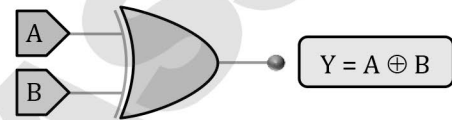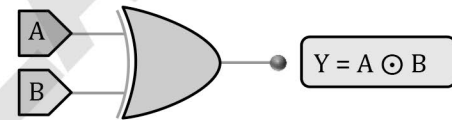**2. XNOR Gate**

Representation :

Boolean expression :  $Y = A \cdot B + \overline{A} \cdot \overline{B}$  or  $Y = A \odot B$





## BEGINNER'S BOX

## ANSWERS KEY

## BEGINNER'S BOX-1

- Value of R should be increased because with the increase in temperature of semiconductor as circuit resistance decreases and current tends to increase.
- $n_e = 5 \times 10^9 \text{ m}^{-3}$
- $n_e = 5 \times 10^{22} \text{ m}^{-3}$ ,  $n_h = 4.5 \times 10^9 \text{ m}^{-3}$
- $n_e/n_h = 6/5$

## BEGINNER'S BOX-2

- (a) 0.2 eV (b) 0.1 eV (c) 0.3 eV
- 200  $\Omega$
- $I_1 = 0$  and  $I = I_2 = 5 \text{ mA}$
- 0.25 A
- (a)  $V_0 = 11.7 \text{ V}$ ,  $I = 2.34 \text{ mA}$  (b)  $V_0 = 11.3 \text{ V}$ ,  $I = 2.26 \text{ mA}$

## BEGINNER'S BOX-3

- (1)
- $I_S = 30 \text{ mA}$ ,  $I_L = 6 \text{ mA}$ ,  $I_Z = 24 \text{ mA}$ ,  $P_Z = 0.144 \text{ W}$
- 40 mA.
- 8671.33  $\text{\AA}$

## BEGINNER'S BOX-4

- $I_C = 6.47 \text{ mA}$ ,  $I_B = 0.13 \text{ mA}$ ,  $\alpha = 0.98$
- 4.93 mA
- 0.53 mA
- $\alpha = 0.98$ ;  $\beta = 49$
- $I_B = 0.1 \text{ mA}$ ;  $I_C = 6.9 \text{ mA}$
- 1 k $\Omega$ ; 185 k $\Omega$
- 1250
- (i) 0.5 mA, (ii) 50 mA, (iii) 5 V